



# DIGITAL CIRCUITS

## Week-7, Lecture-4 Multiplexers

Sneh Saurabh  
14<sup>th</sup> September, 2018




# Digital Circuits: Announcements/Revision

---



---

# Combinational Circuit Design

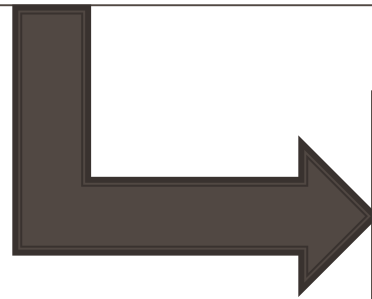

Using Multiplexers



# Multiplexer: Basics

- A multiplexer circuit has a number of data inputs, one or more select inputs, and one output.
- It passes the signal value on one of the data inputs to the output.
- The data input is selected by the values of the select inputs

## 2-to-1 multiplexer:

- Two data inputs, 1 select input and one output
- Output same as the input  $w_0$  if  $s = 0$
- Output same as the input  $w_1$  if  $s = 1$

$$f(s, w_0, w_1) = s'w_0 + sw_1$$

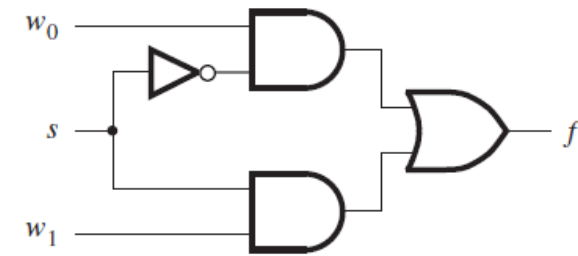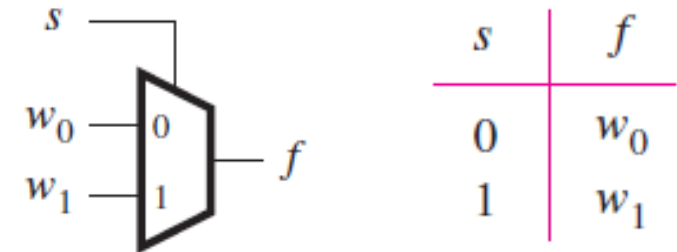


# 4-to-1 Multiplexer

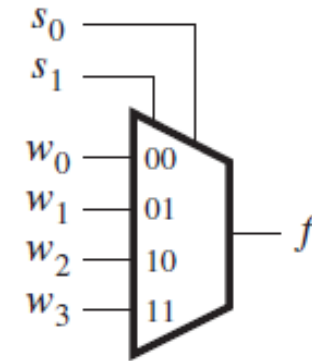
## 4-to-1 multiplexer:

- Four data inputs, 2 select inputs and one output

$$f = s_0's_1'w_0 + s_0s_1'w_1 + s_0's_1w_2 + s_0s_1w_3$$




$s_1$	$s_0$	$f$
0	0	$w_0$
0	1	$w_1$
1	0	$w_2$
1	1	$w_3$

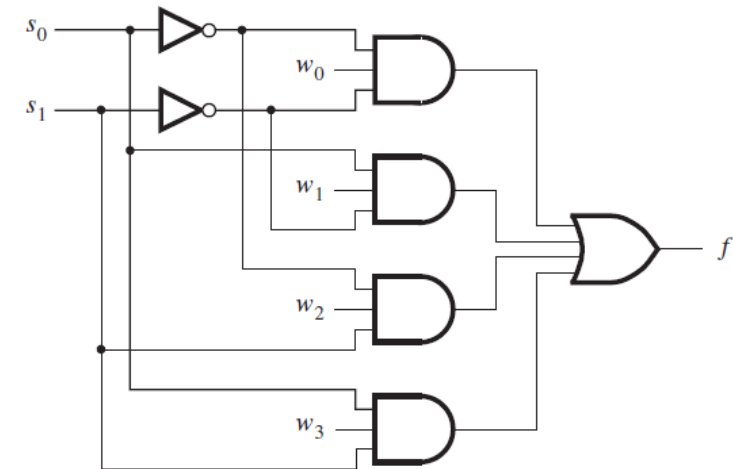

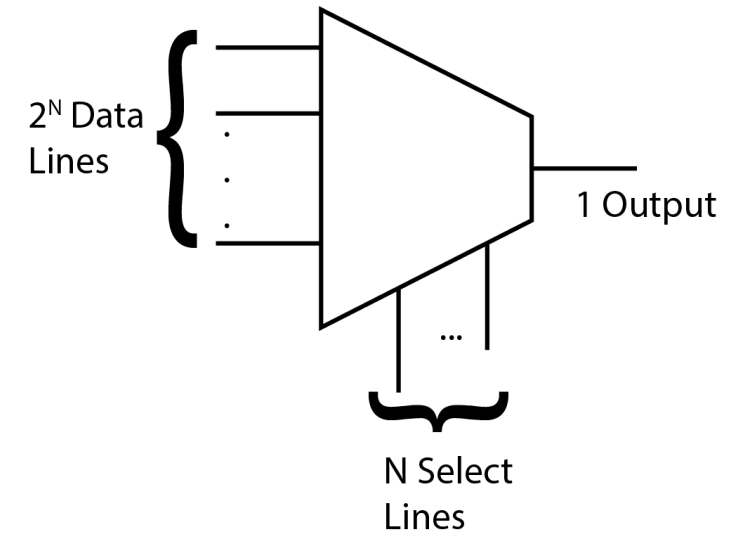
# Large Multiplexer

---


- Similarly larger multiplexers can be built
  - Usually data inputs is  $2^N$ , select inputs are  $N$  and one output
- 
- Larger multiplexers can be built using smaller multiplexors




# 4-to-1 MUX using 2-to-1 MUX

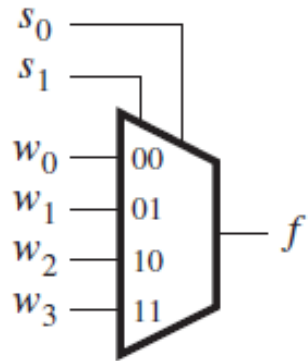
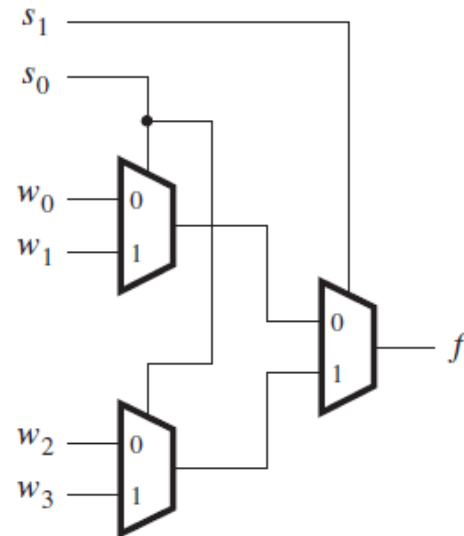
$$f = s_0's_1'w_0 + s_0s_1'w_1 + s_0's_1w_2 + s_0s_1w_3$$
$$= s_1'(s_0'w_0 + s_0w_1) + s_1(s_0'w_2 + s_0w_3)$$



# 16-to-1 MUX using 4-to-1 MUX

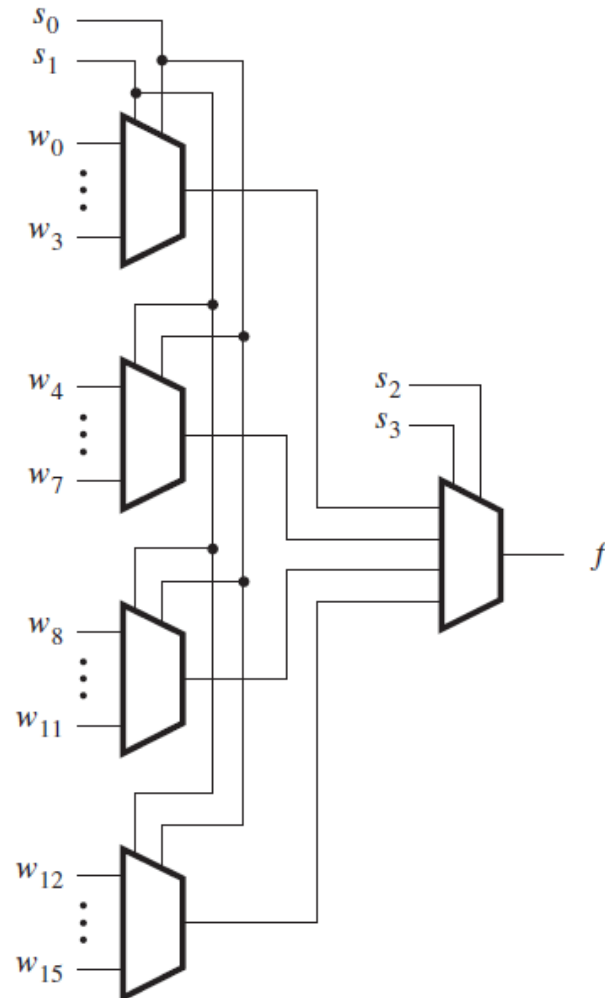

## Practice Problem:

- Verify that the given circuit works as 16-to-1 MUX
- Implement 16-to-1 MUX using only 2-to-1 MUXes
- Implement 16-to-1 MUX using 8-to-1 MUXes and other components as required



# MUX-based implementation using truth table (1)


**Problem:** Given a function (or its truth table) of  $N$  variables, find a MUX-based implementation (using  $2^N$ -to-1 MUX).

**Methodology:**

- The input to a logic function can be used in the select line
- The value of the function corresponding to each row of the truth-table can be specified as data-inputs

**Problem 1:** Given a function  $y = x'$ , find a MUX-based implementation.


$x$	$y$
0	1
1	0

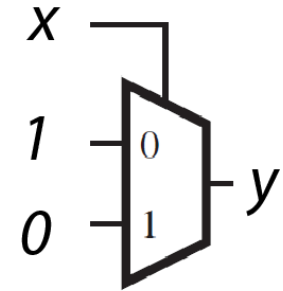

# MUX-based implementation using truth table (2)

**Problem 2:** Given a function  $f = w_1 \oplus w_2$ , find a MUX-based implementation.

$w_1$	$w_2$	$f$
0	0	0
0	1	1
1	0	1
1	1	0

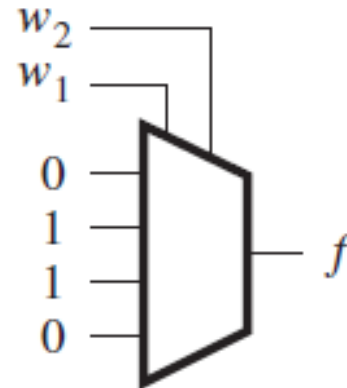


**This is not an efficient implementation**

# MUX-based implementation using truth table (3)

**Problem 3:** Given a function  $f = w_1 \oplus w_2$ , find a **2-to-1 MUX-based** implementation.

$w_1$	$w_2$	$f$		$w_1$	$f$
0	0	0	}	0	$w_2$
0	1	1		1	$\bar{w}_2$
1	0	1	}		
1	1	0			

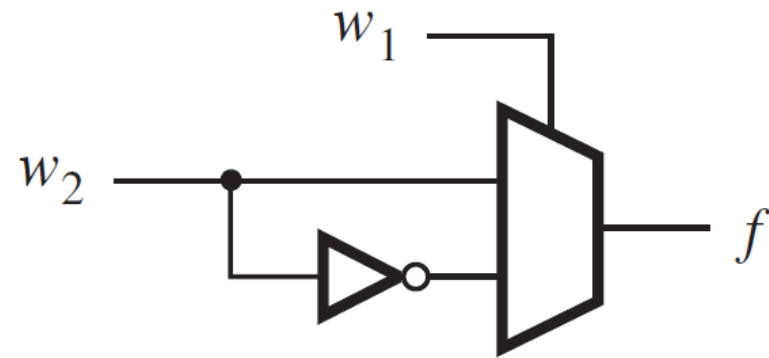


**We will look at a formal way to obtain this implementation**

# MUX-based implementation (4)

**Problem 4:** Given a majority function (truth table shown below), obtain a 4-to-1 MUX-based implementation.

$w_1$	$w_2$	$w_3$	$f$		$w_1$	$w_2$	$w_3$	$f$		$w_1$	$w_2$	$f$	
0	0	0	0	}	0	0	0	0	}	0	0	0	
0	0	1	0		0	0	1	0		0	0	1	$w_3$
0	1	0	0		0	1	0	0		0	1	0	$w_3$
0	1	1	1		0	1	1	1		1	1	1	1
1	0	0	0	}	1	0	0	0	}				
1	0	1	1		1	0	1	1		1			
1	1	0	1		1	1	0	0		1			
1	1	1	1		1	1	1	1		1			

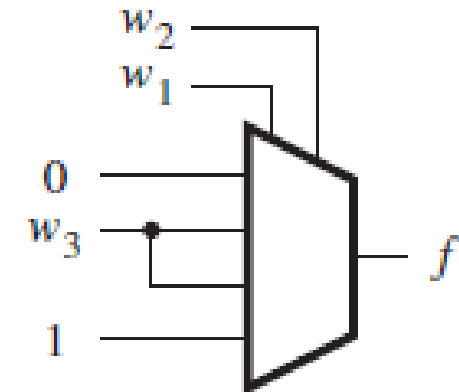

# MUX-synthesis: systematic way



**Claude Shannon (1916 – 2001)**

- American mathematician, electrical engineer, and cryptographer
- Known as "the father of information theory"

# Shannon's Expansion Theorem

## Shannon's Expansion Theorem:

Any Boolean function  $f(w_1, w_2, \dots, w_n)$  can be written in the form:

$$f(w_1, w_2, \dots, w_n) = w_1' \cdot f(0, w_2, \dots, w_n) + w_1 \cdot f(1, w_2, \dots, w_n)$$

- The term  $f(0, w_2, \dots, w_n)$  is known as the cofactor of  $f$  with respect to  $w_1'$
- It is obtained by replacing all occurrences of  $w_1$  in  $f$  with 0
- It is denoted as  $f_{w_1'}$

- The term  $f(1, w_2, \dots, w_n)$  is known as the cofactor of  $f$  with respect to  $w_1$
- It is obtained by replacing all occurrences of  $w_1$  in  $f$  with 1
- It is denoted as  $f_{w_1}$

$$f(w_1, w_2, \dots, w_n) = w_1' \cdot f_{w_1'} + w_1 \cdot f_{w_1}$$

# Shannon's Expansion Theorem: Illustration

## Problem:

Do Shannon's expansion of:  $f = w_1 \oplus w_2$  and implement in terms of 2-to-1 MUX.

## Solution:

$$f = w_1 \oplus w_2 = w_1' \cdot w_2 + w_1 w_2'$$

$$f_{w_1'} = w_2$$

$$f_{w_1} = w_2'$$

$$f = w_1' \cdot f_{w_1'} + w_1 \cdot f_{w_1}$$

