



DIGITAL CIRCUITS

Week-7, Lecture-3 Revision

Sneh Saurabh
13th September, 2018



Digital Circuits: Announcements/Revision



Principles of Logic Optimization: Example

Problem:

Simplify the function: $F(w, x, y, z) = \Sigma m(1, 3, 7, 11, 15)$ which has don't care conditions as: $d(w, x, y, z) = \Sigma m(0, 2, 5)$

Problem:

For the function specified in the previous slide, find the minimized expression for $F'(w, x, y, z)$. Thereafter, find the minimized $F(w, x, y, z)$ in POS form.

$$F'(w, x, y, z) = z' + wy'$$

$$F(w, x, y, z) = z(w' + y)$$


		y			
		00	01	11	10
wz	00	m_0	m_1	m_3	m_2
$w'x'$	00	X	1	1	X
	01	m_4	m_5	m_7	m_6
	01	0	X	1	0
w	11	m_{12}	m_{13}	m_{15}	m_{14}
	11	0	0	1	0
	10	m_8	m_9	m_{11}	m_{10}
	10	0	0	1	0
		z			
		yz			

- Without use of don't care: $F(w, x, y, z) = yz + w'x'z$
- With including X in first row: $F_1(w, x, y, z) = yz + w'x'$
- With including X in m_5 : $F_2(w, x, y, z) = yz + w'z$



7-segment display: Description

7-segment display:

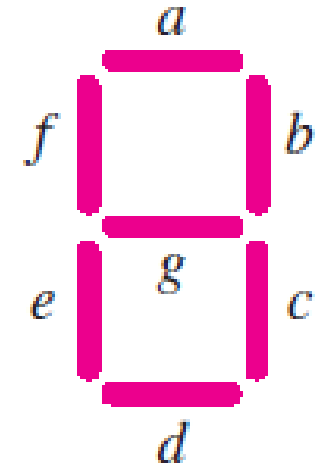- Digit-oriented display
- Seven signals that are used to drive the segments in the display
- Each segment is a small light-emitting diode (LED), which glows when driven by an electrical signal
- The segments are labeled from 'a' to 'g' in the figure



7-segment display: Driver

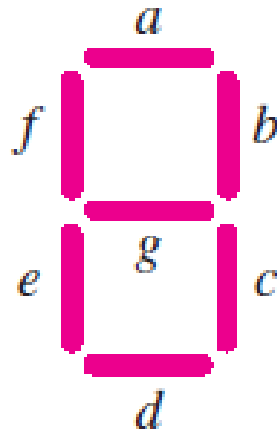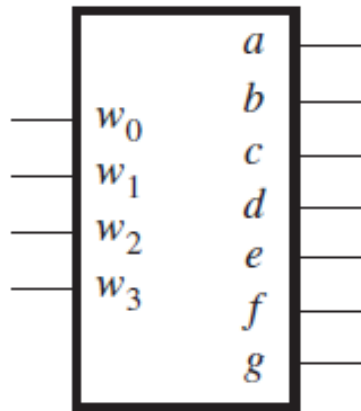

BCD to 7-segment signal

w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

7-segment display: Driver Design

Problem:

Derive minimal sum-of-products expressions for the output a, b, c of the 7-segment display

$w_3 w_2$		$w_1 w_0$			
		00	01	11	10
$w_1 w_0$	00	1	0	1	1
	01	0	1	1	1
	11	X	X	X	X
	10	1	1	X	X

$$a = w_1 + w_3 + w_0 w_2 + w_0' w_2'$$

w_3	w_2	w_1	w_0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

Practice yourself:

$$b = w_0' w_1' + w_0 w_1 + w_2'$$

$$c = w_2 + w_1' + w_0$$

Base of a number system: Problem

Problem:

The first expedition to Mars found only the ruins of a civilization. From the artifacts and pictures, the explorers deduced that the creatures who produced this civilization were four-legged beings with a tentacle that branched out at the end with a number of grasping "fingers". After much study, the explorers were able to translate Martian mathematics. They found the following equation:

$$5x^2 - 50x + 125 = 0$$

with the indicated solutions $x = 5$ and $x = 8$.

The value $x = 5$ seemed legitimate enough, but $x = 8$ required some explanation.

Then the explorers reflected on the way in which Earth's number system developed, and found evidence that the Martian system had a similar history. How many fingers would you say the Martians had?

(From *The Bent of Tau Beta Pi*, Feb 1956)

Base of a number system: Solution

Solution:

Let the base be N .

Therefore, $(50)_N = (5N + 0)_{10}$ and $(125)_N = (1 * N * N + 2N + 5)_{10}$

Given equation is in base N : $5x^2 - 50x + 125 = 0$

Converting this equation to base 10:

$$5x^2 - 5Nx + N^2 + 2N + 5 = 0$$

This equation should hold true for both $x = 5$ and $x = 8$

For $x = 5$

$$125 - 25N + N^2 + 2N + 5 = 0$$

$$N^2 - 23N + 130 = 0$$

$$(N - 13)(N - 10) = 0$$

$$N = 13$$

Checking $x = 8$

$$5 * 64 - 5 * 13 * 8 + 169 + 2 * 13 + 5$$

$$= 320 - 520 + 200 = 0$$