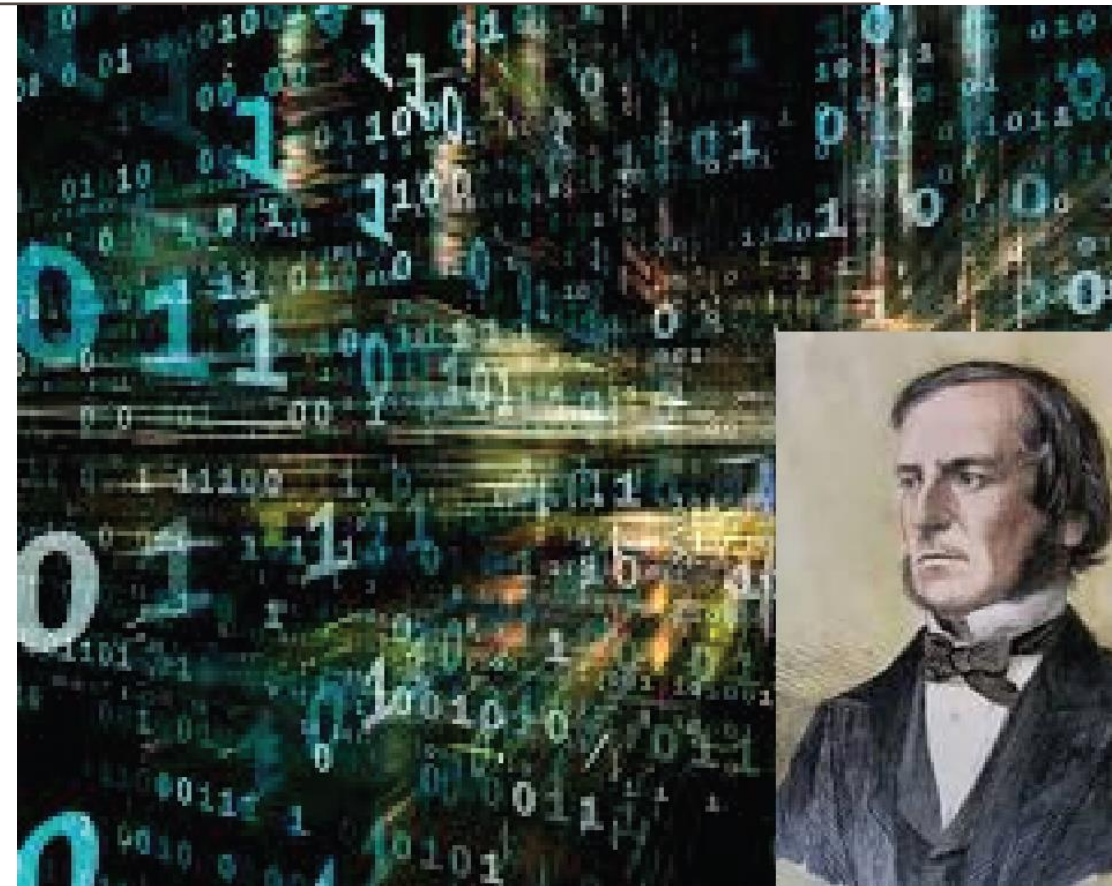





DIGITAL CIRCUITS

Week-2, Lecture-1 Introduction


Sneh Saurabh
7th August, 2018



Digital Circuits: Announcements/Revision

 

Digital Circuits

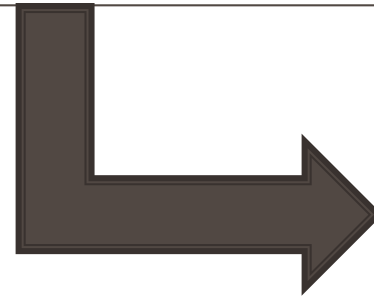


Introduction


Analog System vs. Digital System (4)

- Quality of service
- Maintenance, Flexibility
- Delay (?)

Digital Systems (1)

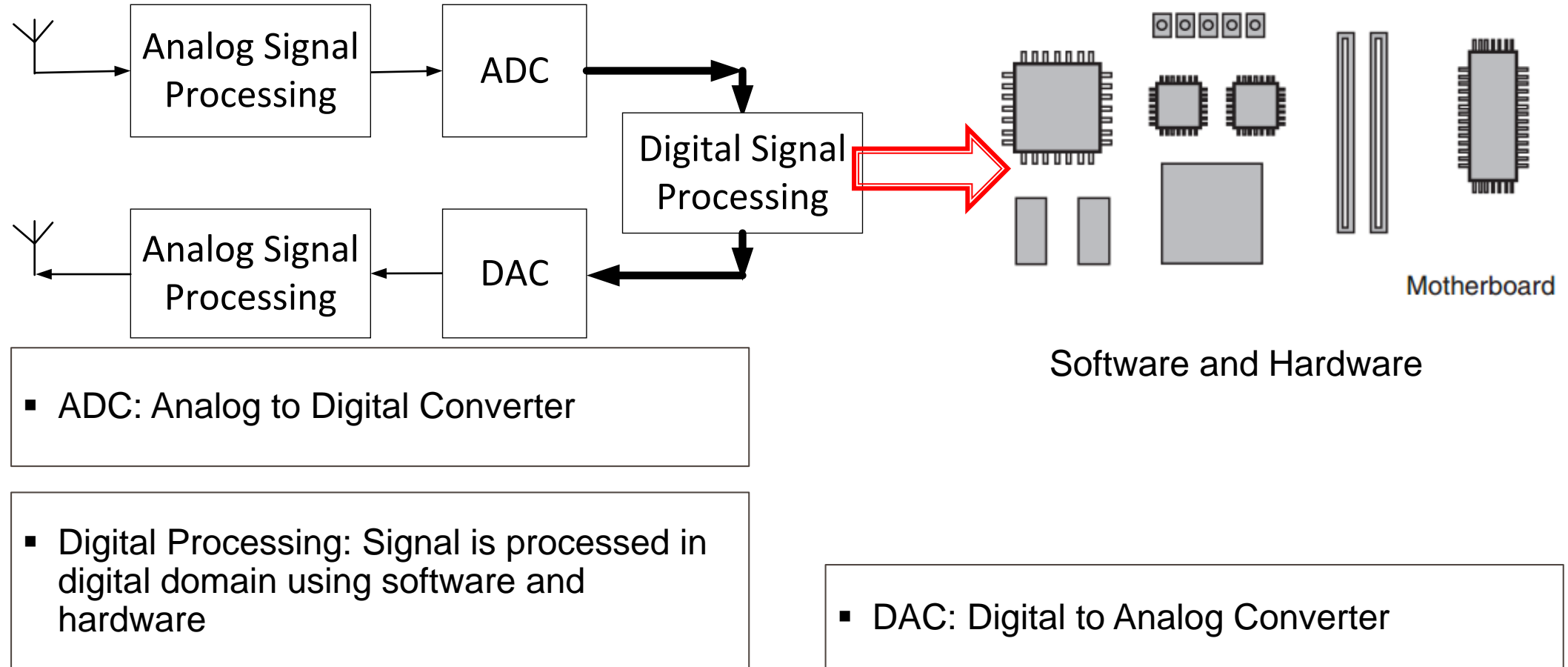


Digital Systems (2)

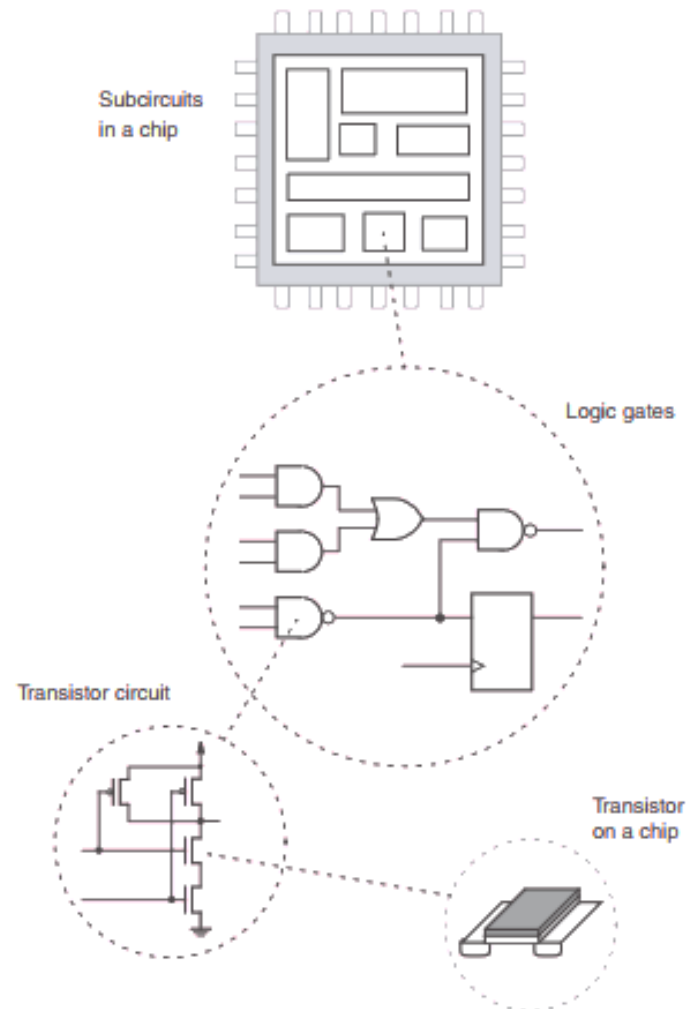

- Digital Systems are realized as chips
- **Chips consists of Logic Gates (often millions of logic gates)**
- Logic gates are made up of transistors


Why Analog Circuits are needed?

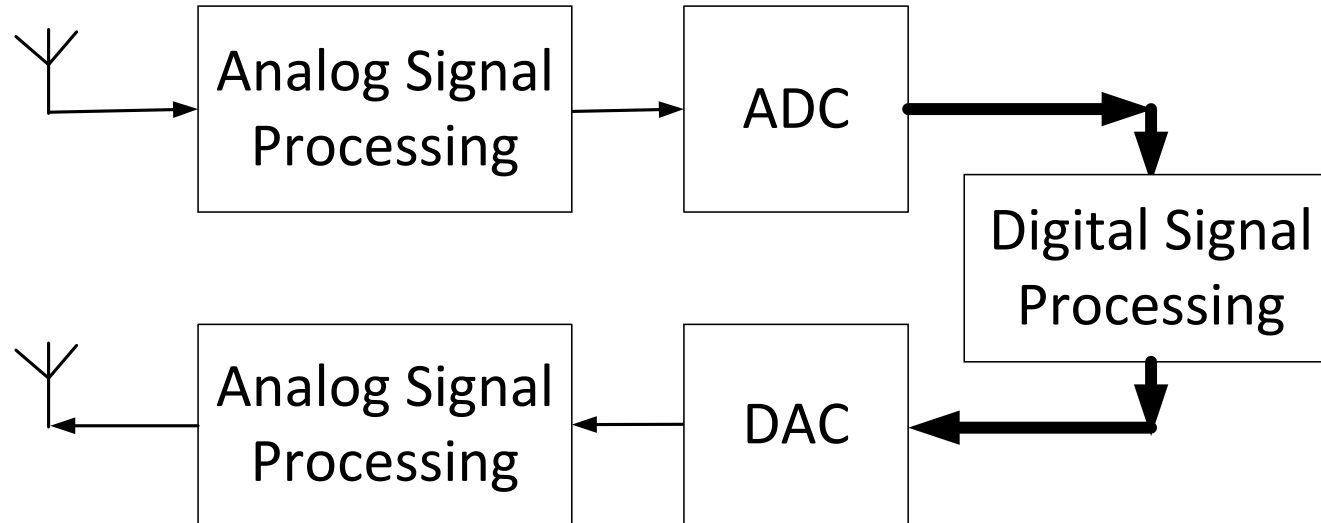

- Analog circuits are important since real signals are analog


- Some initial processing reduces the burden on Digital Signal Processing and overall more-efficient system is realized

Digital Circuits

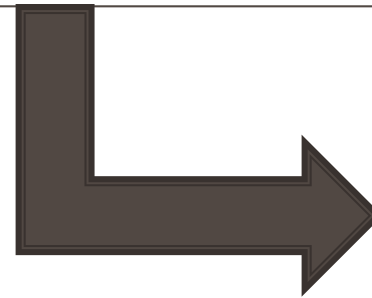

Zeros and
Ones

Digital signals: “Digits”

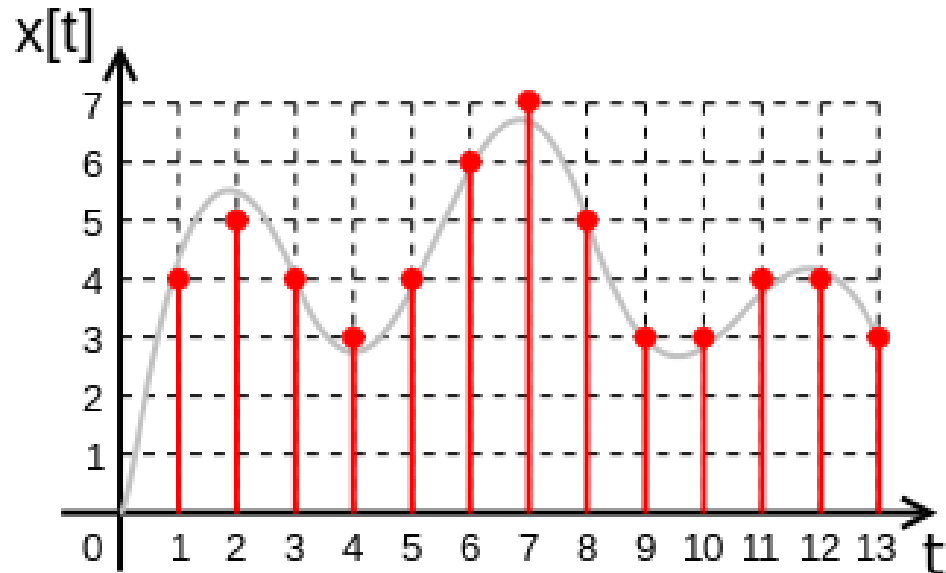

- y can take values from a discrete set of values. For example: $\{0, 1, 2, 3, 4, 5, 6, 7\}$

- In this example, signal is represented as: $\{4, 5, 4, 3, 4, 6, 7, 5, 3, 3, 4, 4, 3, \dots\}$

Why do we call it “Digital” signal?

- Any digital signal is represented in the form of a number or “digits”
- **A number can be represented in many different ways**
- In normal counting we use only “Decimal Numbers”
- Other number systems are possible

Digital signals: Decimal Number

What is a Decimal Number?

- Decimal Number consists of digits {0, 1, 2, 3, 4, 5, 6, 7, 8, 9}
- Decimal Number is said to be in “base 10”
 - Ten digits are used
 - $5723 = 5 \times 10^3 + 7 \times 10^2 + 2 \times 10^1 + 3 \times 10^0$ [Place value of each digit is in power of tens]

Digital signals: Binary Number

- In Digital systems we use “Binary Number”


What is a Binary Number?

- Binary Number consists of digits {0, 1}
- Binary Number is said to be in “base 2”
 - Two digits are used
 - $(1001)_2 = 1 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 9$ [Place value of each digit is in power of two]

Why are Binary Numbers used in Digital System?

- {0, 1} can conveniently be represented as two voltage levels
- Easy to process binary numbers

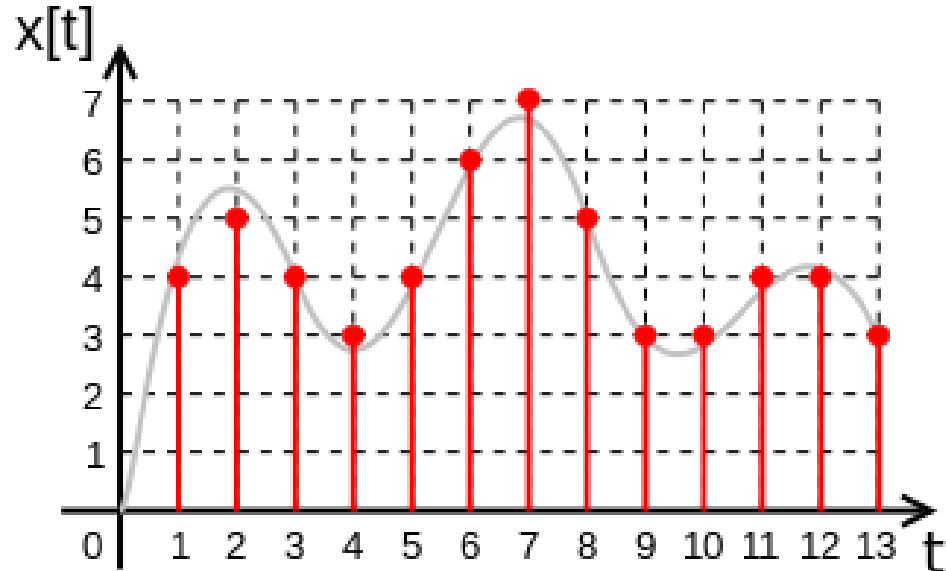Digital signals: In Zeros and Ones (Binary)




- y can take values from a discrete set of values. For example: $\{0, 1, 2, 3, 4, 5, 6, 7\}$

- In this example, signal is represented as: $\{4, 5, 4, 3, 4, 6, 7, 5, 3, 3, 4, 4, 3, \dots\}$

- In this example, signal is represented in Binary number as: $\{100, 101, 100, 011, 100, 110, 111, 101, 011, 011, 100, 100, 011, \dots\}$

In the following lectures we will deal with signals that can take values “0” or “1”

Digital Circuits

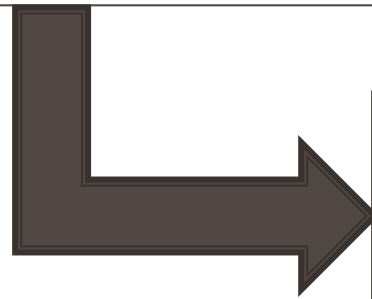


Logic Functions and
Logic Gates

Two states of a Binary Number: Switch



Two states of a switch

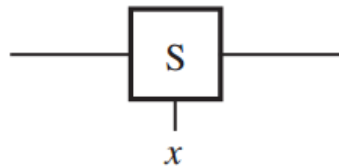


Symbol for a switch

- Two states of a binary number can be represented by a **switch**
 - ON-state and OFF-state

- Assume that the switch is controlled by a variable x
 - If $x = 0$, switch is OFF or “Open”
 - If $x = 1$, switch is ON or “Closed”

Switch/Light bulb: Input/output

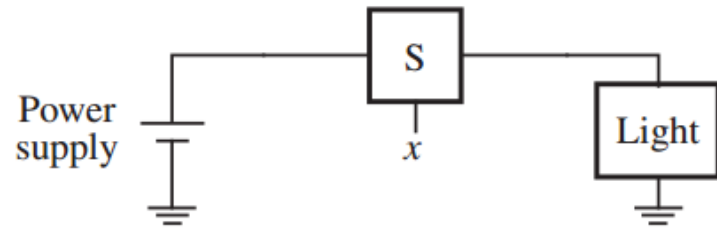


- Switch is used to control Light bulb
- Light bulb glows when current passes through it

- **Light bulb has two states**
 - OFF-state (does not glow) and ON-state (glows)
 - The state of light bulb can be denoted by L
 - OFF-state: $L = 0$
 - ON-state: $L = 1$

- Switch is used to control the state of Light bulb
- In this system:
 - Input: switch variable x
 - Output: state of the light bulb L

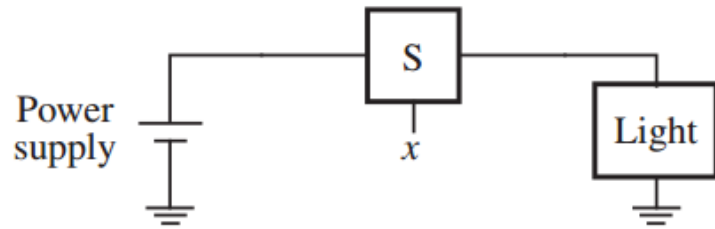Logic function: relationship between Input/output




- Derive a relationship between Input and Output

- When $x = 0$, then $L = 0$
- When $x = 1$, then $L = 1$

- $L = x$ is the relationship between the input and the output
- $L(x) = x$
- $L(x)$ is a **logic function**
- x is the **input variable**

Logic function: AND function

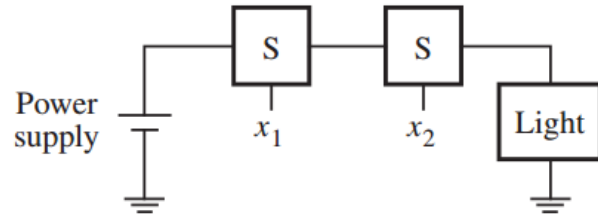


- Inputs are: (x_1, x_2)
- Output is: L
- Derive a relationship between Input and Output

- The light bulb will glow if switch “ x_1 **and** x_2 ” are closed
- $L = 1$ if $x_1 = 1$ **and** $x_2 = 1$, $L = 0$ otherwise
- $L(x_1, x_2) = x_1 . x_2$

- Symbol “.” is known as **AND operator** and is said to implement logical **AND** function

Logic function: OR function

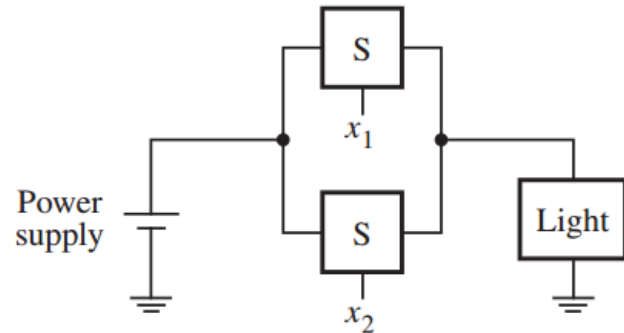


- Inputs are: (x_1, x_2)
- Output is: L
- Derive a relationship between Input and Output

- The light bulb will glow if switch “ x_1 **or** x_2 ” are closed
- $L = 1$ if $x_1 = 1$ **or** $x_2 = 1$ **or** $x_1 = x_2 = 1$, $L = 0$ if $x_1 = x_2 = 0$
- $L(x_1, x_2) = x_1 + x_2$

- Symbol “+” is known as **OR operator** and is said to implement logical **OR** function

Logic function: Complex Logic

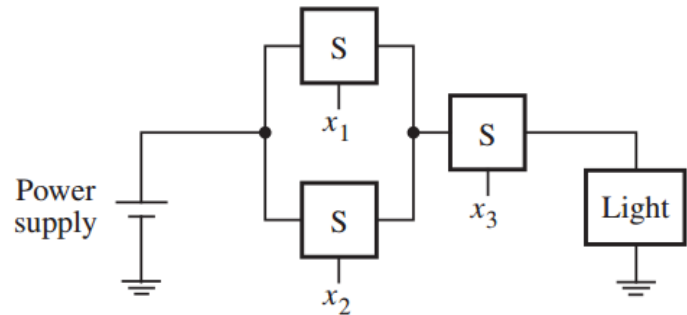
- AND and OR operations can be used to implement complex logic circuit/function/expression



- The light bulb will glow if switch “(x_1 **or** x_2) and x_3 ” are closed
- $L(x_1, x_2, x_3) = (x_1 + x_2) \cdot x_3$

- Inputs are: (x_1, x_2, x_3)
- Output is: L
- Derive a relationship between Inputs and Output

Logic function: Inversion/Complement/NOT

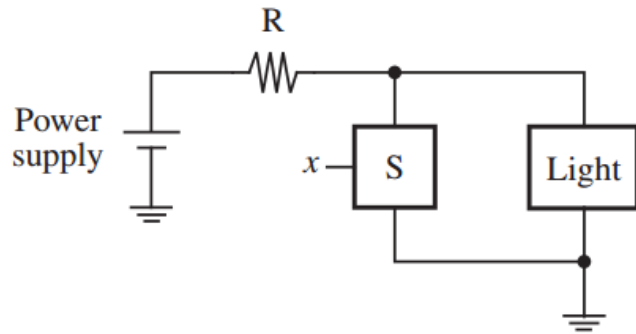

- Switch is connected in parallel with the light

- Current always flow through “**low resistance path**”

- Switch has **infinite resistance** when “OPEN”
- Switch has **zero resistance** when “CLOSED”

- Light bulb has some **finite resistance**

- When $x = 0$, then $L = 1$
- When $x = 1$, then $L = 0$

- $L = \bar{x} = x' = !x = \sim x$
- L is the complement of x
- This is also known as **NOT** operation
- x is the **input variable**

Truth Table (1)

- Logic operations can also be defined in form of a table
- These tables are known as **Truth Tables**

x	\bar{x}
0	1
1	0

x_1	x_2	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

Truth Table (2)

For 3 *variable* inputs, how many entries will be there in the truth table?

x_1	x_2	x_3	$x_1 \cdot x_2 \cdot x_3$	$x_1 + x_2 + x_3$
0	0	0	0	0
0	1	0	0	1
1	0	0	0	1
1	1	0	0	1
0	0	1	0	1
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

Truth Table (3)

Question:

For N *variable* inputs, how many entries will be there in the truth table?

Answer:

Each input can take 2 values (0 and 1).

Total possibilities:

$$2 \times 2 \times 2 \dots N \text{ times} = 2^N$$

Inference:

- The number of entries increases exponentially with N
- Truth table representation of a function is feasible for small N
- For large N truth table representation will be too big and not feasible
- Other representations such as logic expression is more compact for large N