 





DIGITAL CIRCUITS

Week-2, Lecture-2 Introduction


Sneh Saurabh
8th August, 2018



Digital Circuits: Announcements/Revision

 

Digital Circuits

 

Logic Functions and
Logic Gates

Logic Expression: Precedence of Operators

- $()$: Bracket
- NOT
- AND
- OR

- What will be the order of computation for the following expression:

$$f(x_1, x_2, x_3) = \overline{x_1} \cdot (x_2 + x_3 \cdot x_1)$$

- Computation 1: Bracket
 - $x_3 \cdot x_1$ AND
 - $x_2 + x_3 \cdot x_1$ OR
- Computation 2: $\overline{x_1}$ NOT
- Computation 3: $\overline{x_1} \cdot (x_2 + x_3 \cdot x_1)$ AND

Logic function: Complement of a function

- Complement can be defined for complex function also
- $f(x_1, x_2) = (x_1 + x_2)$
- $\bar{f}(x_1, x_2) = \overline{(x_1 + x_2)}$

- NOT of OR is known as NOR operation
- Similarly NOT of AND operation is known as NAND operation




- Find the truth table for this function

x_1	x_2	$f(x_1, x_2)$ $= x_1 + x_2$	$\bar{f}(x_1, x_2)$ $= \overline{(x_1 + x_2)}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0


Logic gates: AND, OR, NOT (Basic Gates)

What is a *Logic Gate*?

   
- Hardware implementation of logic operation such as NOT, AND, OR, NAND, NOR etc. in terms of transistors etc. is known as **Logic Gate**
- A logic gate has one or more inputs and only one output
- Output depends on the value of inputs
- Convenient to represent in terms of schematic
- A bubble at the input or the output denotes taking complement



Logic gates: NAND, NOR

 





NAND

 

NOR

- NAND/NOR gates are widely used because it is easy to realize/fabricate them using transistors
-
- AND/OR/NOT gates can be realized using only NAND gates
 - AND/OR/NOT gates can also be realized using only NOR gates
 - NAND/NOR gates are called ***universal gates***


NAND, NOR: Universal gates

    


A	B	X	Y	Q
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1

Similarly, it can be shown that NOT, OR, AND operation can be realized using NOR gates alone

Logic gates: XOR, XNOR

 

x_1	x_2	$XOR(x_1, x_2) = x_1 \oplus x_2$
0	0	0
0	1	1
1	0	1
1	1	0

 

x_1	x_2	$XNOR(x_1, x_2) = \overline{x_1 \oplus x_2}$
0	0	1
0	1	0
1	0	0
1	1	1

Positive and Negative Logic

- Logic Gates are designed in terms of voltage levels
 - Two levels are defined: H (High) and L (Low)
- The **interpretation** of these voltages in terms of “0” and “1” can be in two ways

Positive Logic:

- H (High) is “1” and L (Low) is “0”


x_1	x_2	$f(x_1, x_2)$
0	0	0
0	1	0
1	0	0
1	1	1



Negative Logic:

- H (High) is “0” and L (Low) is “1”

x_1	x_2	$f(x_1, x_2)$
1	1	1
1	0	1
0	1	1
0	0	0

 


x_1	x_2	$f(x_1, x_2)$
L	L	L
L	H	L
H	L	L
H	H	H

Triangles indicate negative logic

Negative Logic system is rarely used, and we will assume positive logic system in this course

Logic Network or Logic Circuit

 
- NOT, AND, OR gates can be used to implement any logic function
- A complex logic function is implemented by interconnecting logic gates



- **Logic Network** or **Logic Circuit** is an interconnection of logic gates

- Same Logic Function can be implemented by different Logic Networks
- A designer task is to find a Logic Network with less complexity (less number of gates)

Tasks for a Logic Circuit Designer

 


Analysis:

- Given a logic network, determine the **logic function** that is implemented

Synthesis:

- Given a logic function, find a **logic network** that implements it
- There are many solutions, choose the best

 Logic Network Analysis: Function $f(x_1, x_2)$



Analysis: Find the function that is represented by the above Logic Network

Approach:

a) Write the Logic Function

b) Write the Truth Table


Logic Function:

$$A = \overline{x_1} \quad B = x_1 \cdot x_2$$

$$f(x_1, x_2) = \overline{x_1} + x_1 \cdot x_2$$

x_1	x_2	A	B	$f(x_1, x_2)$
0	0	1	0	1
0	1	1	0	1
1	0	0	0	0
1	1	0	1	1

Logic Network Analysis: Timing Diagram

 

Timing Diagram: Changes in signals at different point of time represented graphically.

x_1	x_2	A	B	$f(x_1, x_2)$
0	0	1	0	1
0	1	1	0	1
1	0	0	0	0
1	1	0	1	1

Assumption: output of a gate changes instantaneously when its input changes

