



DIGITAL CIRCUITS

Week-6, Lecture-4
K-map


Sneh Saurabh
7th September, 2018



Digital Circuits: Announcements/Revision



Digital Circuits

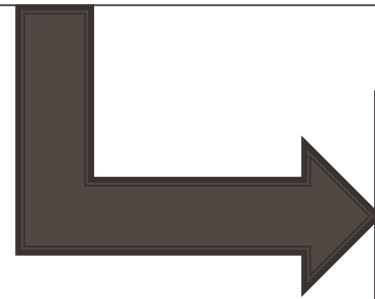

Combinational Circuit Design

K-Map: Bigger combination, fewer literals

- The number of adjacent squares that may be combined must always represent a number that is a power of two, such as 1, 2, 4, and 8 [otherwise number of literals will not reduce]
- As more adjacent squares are combined, we obtain a product term with fewer literals

For three variables function:

- One square represents one minterm, giving a term with three literals
- Two adjacent squares represent a term with two literals
- Four adjacent squares represent a term with one literal
- Eight adjacent squares encompass the entire map and produce a function that is always equal to 1

K-Map: Three variables simplification (reuse squares)

Simplify $F(x, y, z) = \Sigma m(0, 2, 4, 5, 6)$

- First represent the given function on K-map

- Find possible adjacent squares:

- m_0, m_2, m_4 and m_6 : $= z'$
- m_4 and m_5 : $= xy'z' + xy'z = xy'$

$$f(x, y, z) = z' + xy'$$

- The same square is allowed to be combined multiple times (in different combinations)
- It is better to combine squares than leave it isolated (combination reduces number of literals)

		y			
		00	01	11	10
x	0	m_0 $x'y'z'$	m_1 $x'y'z$	m_3 $x'yz$	m_2 $x'yz'$
	1	m_4 $xy'z'$	m_5 $xy'z$	m_7 xyz	m_6 xyz'

		y			
		00	01	11	10
x	0	m_0 1	m_1	m_3	m_2 1
	1	m_4 1	m_5 1	m_7	m_6 1


Note: $y'z' + yz' = z'$

K-Map: Three variables simplification (from SOP)

Problem: $F(A, B, C) = A'C + A'B + AB'C + BC$

- Express the above function as a sum of minterms
 - Find the minimal sum-of-products expression
- First represent the given function on the K-map
 - Mark 1 in K-map corresponding to each product term
 - Product term is identified on K-map by intersection of literals
- Given K-map, expressing a function in minterm is straightforward
 - $F(A, B, C) = \Sigma m(1, 2, 3, 5, 7)$
- Combine squares:
 - m_1, m_3, m_5 and m_7 : C
 - m_3 and m_2 : $A'B$

▪ $F(A, B, C) = A'B + C$

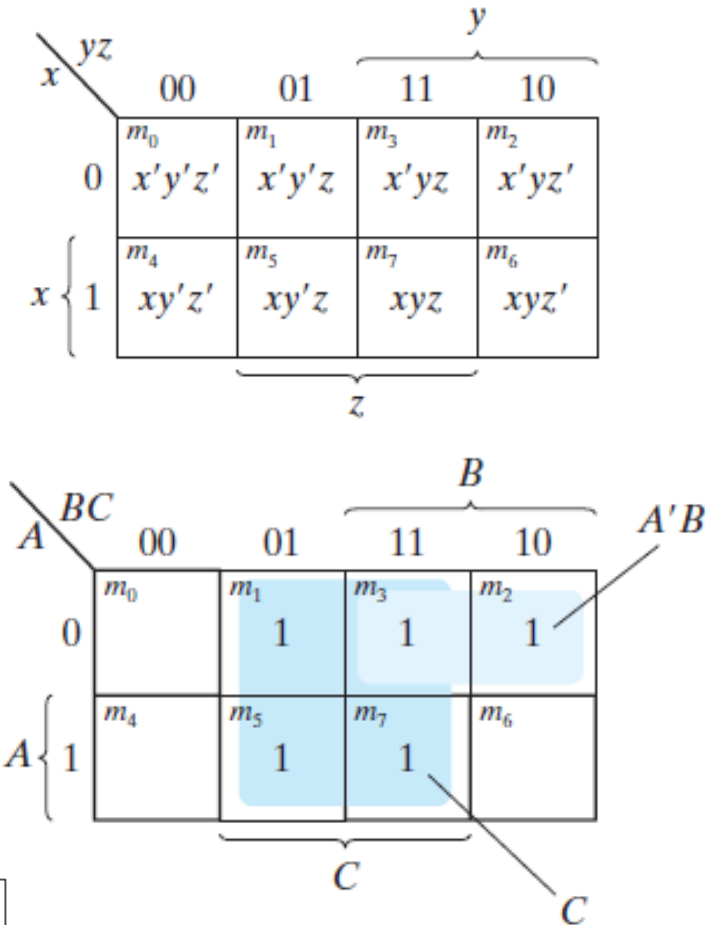

K-Map: Four variables

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

		y			
		00	01	11	10
wx	00	m_0 $w'x'y'z'$	m_1 $w'x'yz'$	m_3 $w'x'yz$	m_2 $w'x'yz'$
	01	m_4 $w'xy'z'$	m_5 $w'xyz'$	m_7 $w'xyz$	m_6 $w'xyz'$
	11	m_{12} $wxy'z'$	m_{13} $wxy'z$	m_{15} $wxyz$	m_{14} $wxyz'$
	10	m_8 $wx'y'z'$	m_9 $wx'yz'$	m_{11} $wx'yz$	m_{10} $wx'yz'$

- Four variables:

➤ Sixteen minterms: 16 squares

- Rows/columns are arranged as Gray code

➤ Only one bit changes in value from one adjacent column/row to the next

- Minterm corresponding to each square is obtained by concatenation of row-number and column-number

➤ Example: Consider square in second row, third column m_7 : row is 01 and column is 11

K-Map: Four variables minimization

		y			
		00	01	11	10
wx	00	m_0 $w'x'y'z'$	m_1 $w'x'y'z$	m_3 $w'x'yz$	m_2 $w'x'yz'$
	01	m_4 $w'xy'z'$	m_5 $w'xy'z$	m_7 $w'xyz$	m_6 $w'xyz'$
	11	m_{12} $wxy'z'$	m_{13} $wxy'z$	m_{15} $wxyz$	m_{14} $wxyz'$
	10	m_8 $wx'y'z'$	m_9 $wx'y'z$	m_{11} $wx'yz$	m_{10} $wx'yz'$

Diagram labels: w (vertical axis), x (horizontal axis), z (bottom axis), y (top axis).

- Procedure similar as for three variables
 - Combine adjacent squares to get rid of literals
- K-map is considered to lie on a surface with:
 - top and bottom edges touch each other to form adjacent squares
 - right and left edges touch each other to form adjacent squares
 - m_3 and m_{11} are adjacent
 - m_{12} and m_{14} are adjacent

K-Map: Bigger combination, fewer literals

For four variables function:

- One square represents one minterm, giving a term with four literals
- Two adjacent squares represent a term with three literals
- Four adjacent squares represent a term with two literals
- Eight adjacent squares represent a term with one literal
- Sixteen adjacent squares encompass the entire map and produce a function that is always equal to 1

K-Map: Four variables simplification

Simplify: $F(w, x, y, z) = \Sigma m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$

- First represent the given function on K-map

		y			
		00	01	11	10
w	00	m_0 $w'x'y'z'$	m_1 $w'x'y'z$	m_3 $w'x'yz$	m_2 $w'x'yz'$
	01	m_4 $w'xy'z'$	m_5 $w'xy'z$	m_7 $w'xyz$	m_6 $w'xyz'$
	11	m_{12} $wxy'z'$	m_{13} $wxy'z$	m_{15} $wxyz$	m_{14} $wxyz'$
	10	m_8 $wx'y'z'$	m_9 $wx'y'z$	m_{11} $wx'yz$	m_{10} $wx'yz'$

		y			
		00	01	11	10
w	00	m_0 1	m_1 1	m_3	m_2 1
	01	m_4 1	m_5 1	m_7	m_6 1
	11	m_{12} 1	m_{13} 1	m_{15}	m_{14} 1
	10	m_8 1	m_9 1	m_{11}	m_{10}

Note: $w'y'z' + w'yz' = w'z'$
 $xy'z' + xyz' = xz'$

- Find possible adjacent squares:

- $m_0, m_1, m_4, m_5, m_{12}, m_{13}, m_8$ and $m_9 := y'$
- m_2, m_6, m_0 and $m_4 := w'z'$
- m_6, m_{14}, m_4 and $m_{12} := xz'$

$$f(x, y, z) = y' + w'z' + xz'$$

K-Map: Four variables simplification (from SOP)

Problem:

Simplify the Boolean function

$$F(A, B, C, D) = A'B'C' + B'CD' + A'BCD' + AB'C'$$


- First represent the given function on the K-map

- $A'B'C'$: m_0 and m_1 , $B'CD'$: m_2 and m_{10}
- $A'BCD'$: m_6 $AB'C'$: m_8 and m_9

- Combine squares:


- m_0, m_1, m_8 and m_9 : $B'C'$
- m_0, m_2, m_8 and m_{10} : $B'D'$
- m_2 and m_6 : $A'CD'$

- $F(A, B, C) = B'C' + B'D' + A'CD'$**

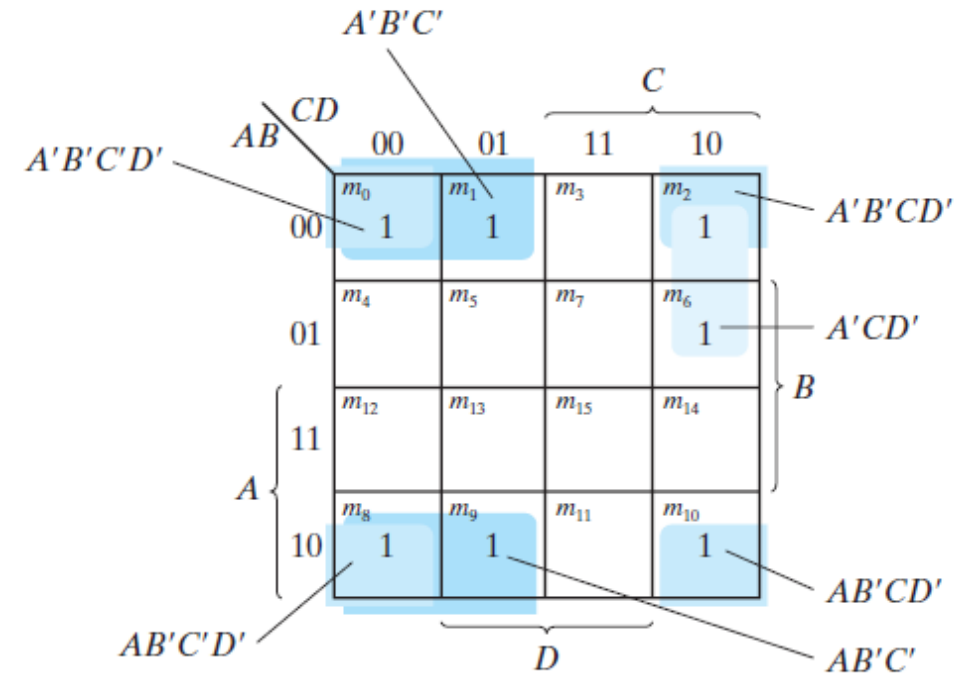

Note: $A'B'C'D' + A'B'CD' = A'B'D'$
 $AB'C'D' + AB'CD' = AB'D'$
 $A'B'D' + AB'D' = B'D'$
 $A'B'C' + AB'C' = B'C'$

K-Map: Five variables

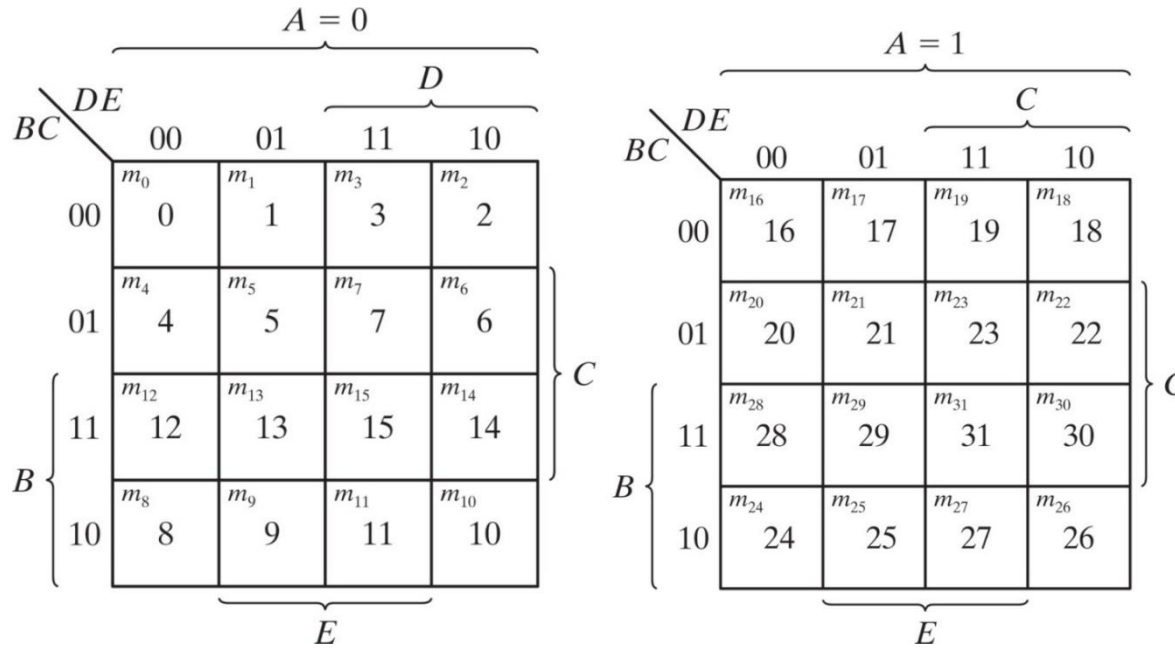

- Five variables: 32 minterms: 32 squares

- Two four-variable K-maps can be used to represent the function
- Two K-maps differ by one variable: $A = 0$ and $A = 1$
 - Minterms m_0 to m_{15} : belong to $A = 0$
 - Minterms m_{16} to m_{31} : belong to $A = 1$


- Each four-variable K-map retains the previously defined adjacency when taken separately
- Each square in $A = 0$ K-map is adjacent to corresponding square in $A = 1$ K-map
 - $(m_4$ and $m_{20})$, $(m_{15}$ and $m_{31})$,

K-Map: Five variables representation


Simplify:

$$F(A, B, C, D, E) = \sum m(0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$$

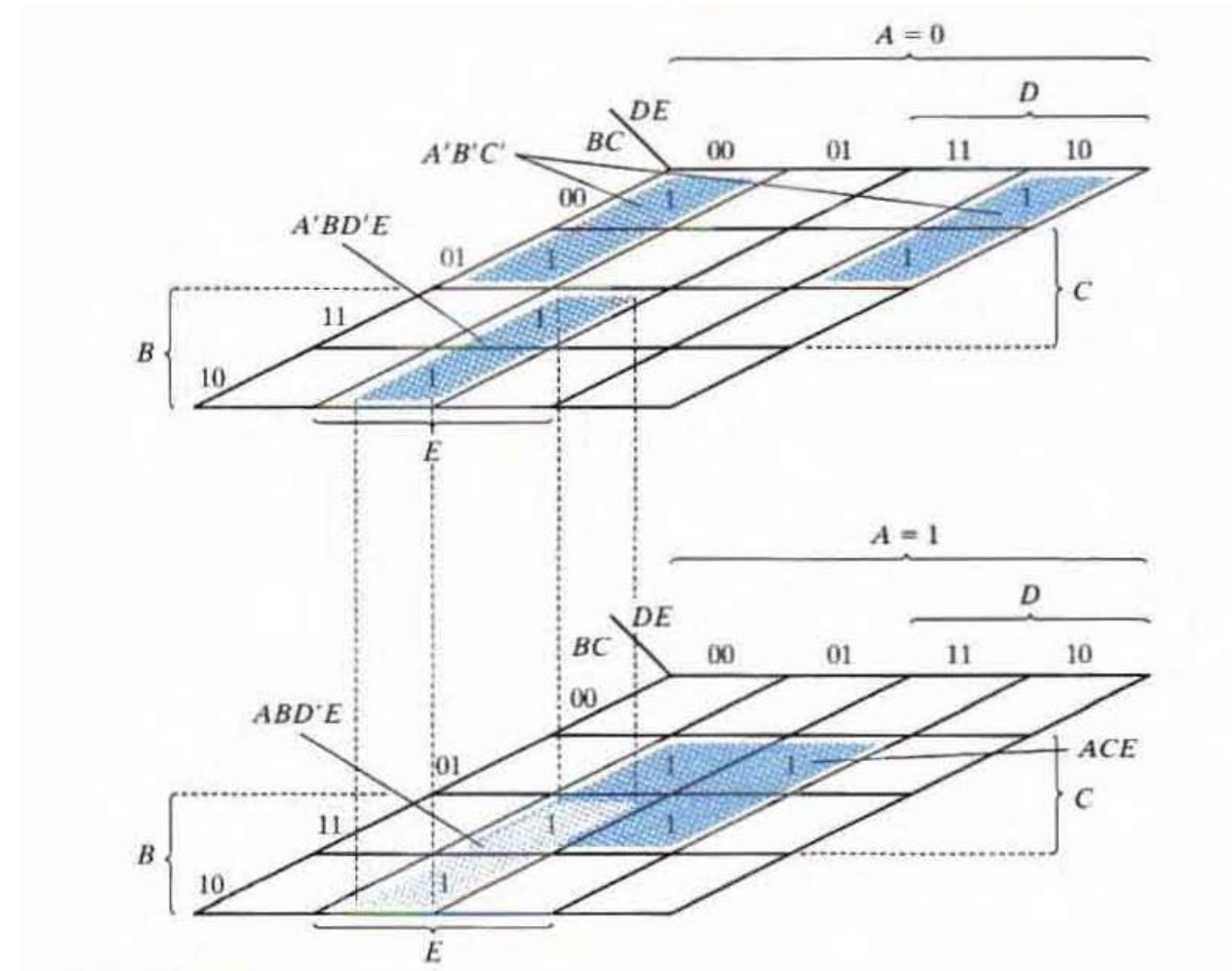- First represent the given function on the K-map
- Minterms m_0 to m_{15} : belongs to $A = 0$: Six terms
- Minterms m_{16} to m_{31} : belongs to $A = 1$: Five Terms



K-Map: Five variables simplification

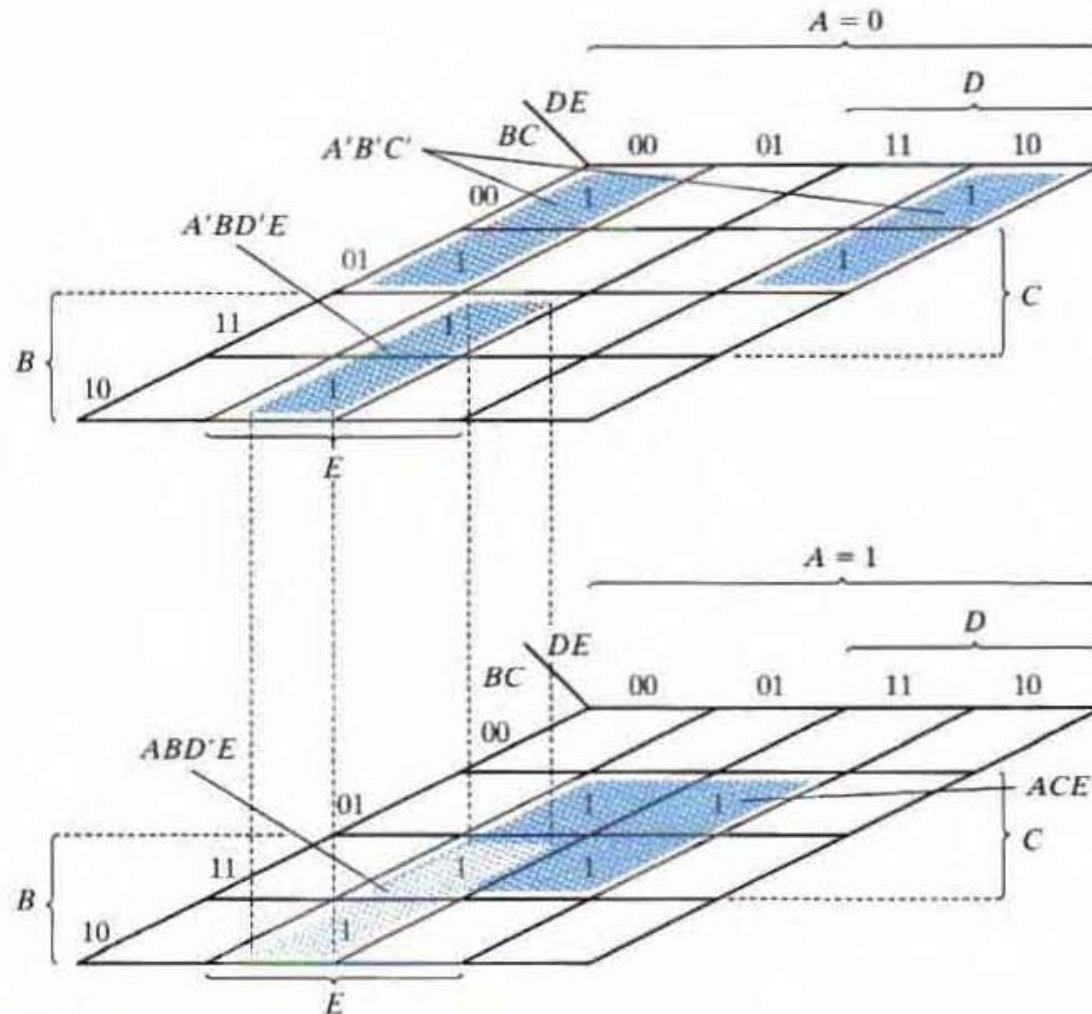

- Find possible adjacent squares
- Four squares in $A = 0$ are combined: $A'B'E'$
- Four squares in the last two rows in both $A = 0$ and $A = 1$ can be combined: $BD'E$
- Four squares in the center for $A = 1$: ACE

$$f(A, B, C, D, E) = A'B'E' + BD'E + ACE$$