



DIGITAL CIRCUITS

Week-13, Lecture-2 Sequential Circuits

Sneh Saurabh
9th November, 2018



Digital Circuits: Announcements/Revision



Sequential Circuits



Design

Sequential Circuit Design: Optimized Implementation


- With the following implementation, what would be the next state for the invalid states:

➤ $T_A = P_C'P_B$

➤ $T_B = P_A + P_B'P_C$

➤ $T_C = P_BP_C + P_B'P_C'$

 First find T_A, T_B and T_C and then N_A, N_B and N_C





If the counter enters an invalid state, it remains in the invalid state for ever!

How to avoid this?

Present State			Next State			Flip-flop inputs		
P_A	P_B	P_C	N_A	N_B	N_C	T_A	T_B	T_C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	1	0	1	0
0	1	0	1	1	0	1	0	0
0	1	1	0	1	0	0	0	1
1	0	0	1	1	1	0	1	1
1	0	1	1	1	1	0	1	0
1	1	0	0	0	0	1	1	0
1	1	1	1	0	0	0	1	1

Sequential Circuit Design: Avoiding being stuck

  - Just use reset
- Design such that FSM eventually transitions to a valid state
 - May limit exploiting don't care states



Sequential Circuit Design: State Reduction

- Reduction in the number of flip-flops
- Involves reduction in the number of states in the state table without changing the input/output behaviour

- Resource required in realizing next state logic and output logic: effect of reducing the number of flip-flops unpredictable

- Since m flip-flops realize 2^m states, reduction in the number of states may not lead to reduction in flip-flops

- Example: number of states reduce from 14 to 9, still 4 flip-flops will be required

- Example: number of states reduce from 10 to 6, number of flip-flops reduced from 4 to 3

Sequential Circuit Design: State Reduction Algorithm

- **Algorithm:** Two states are said to be **equivalent** if, for each member of the set of inputs, they give exactly the same output and send the circuit either to the same state or to an equivalent state.

- When two states are equivalent, one of them can be removed without altering the input-output relationships.

Problem 1:

Reduce the number of states in the state table shown alongside

- Find two present states that go to the same next state and have the same output for both input combinations
- e and g are equivalent states

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

Sequential Circuit Design: State Reduction Algorithm


- Find two present states that go to the same next state and have the same output for both input combinations
- d and f are equivalent states

- Number of states reduced from 7 to 5

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

 Sequential Circuit Design: Sequence Detector



- x is input bits coming in sequence
- $x = 10111000111010111 \dots$
- y is output indicating whether a given (target) sequence was detected
- $y = 00000000010001 \dots$
- y bit is 1 when a given (target) sequence is detected

Sequence Detector: Overlapping vs. Non-overlapping

Detection of target sequence can be defined in two ways:

1. **Overlapping sequence:** the final bits of one sequence can be the start of another sequence
2. **Non-overlapping sequence:** two matched sequences have all bits different

Example: Given sequence is 11011

Assume x is 11011011011.

What would be the output for a) overlapping sequence
b) non-overlapping sequence?

Answer:

a) If it is overlapping: y is 00001001001

b) If it is non-overlapping: 00001000001

Sequence detector can be implemented as either Moore or Mealy FSM

Sequence Detector: Non-overlapping

Problem 2: Draw the state diagram for an FSM that detects a non-overlapping sequence **1010**

- a) First draw the transitions that correspond to correct sequence
- b) Draw the transitions that break the sequence
- c) Draw transition from the final state

Define states based on bits that have matched (take the maximal length):


$S_0 = '0'$

$S_1 = '1'$

$S_2 = '10'$



$S_3 = '101'$

$S_4 = '1010'$

 



Sequence Detector: Non-overlapping

  b) Draw the transitions that break the sequence



Sequence Detector: Non-overlapping

 
 
c) Draw the transition from the final state



Sequence Detector: Overlapping


Problem 3: Draw the state diagram for an FSM that detects a overlapping sequence **1010**

  c) Draw the transition from the final state



Sequence Detector: Mealy Machine (1)

 Problem 3: Draw the state diagram for an FSM that detects a overlapping sequence **1010**. The machine should be **Mealy Type**.



State	Inputs		Output
	0	1	
S_0	S_0	S_1	0
S_1	S_2	S_1	0
S_2	S_0	S_3	0
S_3	S_4	S_1	0
S_4	S_0	S_3	1

State	Inputs	
	0	1
S_0	$S_0/0$	$S_1/0$
S_1	$S_2/0$	$S_1/0$
S_2	$S_0/0$	$S_3/0$
S_3	$S_4/1$	$S_1/0$
S_4	$S_0/0$	$S_3/0$

Sequence Detector: Mealy Machine (2)

State Reduction: Possible in *Mealy Machine*

State	Inputs	
	0	1
S_0	$S_0/0$	$S_1/0$
S_1	$S_2/0$	$S_1/0$
S_2	$S_0/0$	$S_3/0$
S_3	$S_4/1$	$S_1/0$
S_4	$S_0/0$	$S_3/0$

State	Inputs	
	0	1
S_0	$S_0/0$	$S_1/0$
S_1	$S_2/0$	$S_1/0$
S_2	$S_0/0$	$S_3/0$
S_3	$S_2/1$	$S_1/0$

- The Mealy Machine requires one less state than the corresponding Moore Machine
- Mealy Machines make use of inputs also when computing the output.

Digital Circuits: Practice Problems

Problems 6.11-6.30

from “Digital Design”– M. Morris Mano & Michael D. Ciletti, Ed-5, Pearson (Prentice-Hall).

