



# DIGITAL CIRCUITS

## Week-12, Lecture-1 Sequential Circuits

Sneh Saurabh  
30<sup>th</sup> October, 2018




# Digital Circuits: Announcements/Revision

---



---


# Sequential Circuits

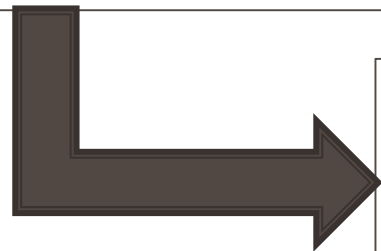

## Registers and Counters
 
# Binary Counter with Parallel Load: Operation


- **Parallel Load:** used for transferring an initial binary number into the counter prior to the count operation.



Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

- When *Clear* = 0, the counter is cleared regardless of the presence other inputs (it is asynchronous)
- When *Load* = 1, data from *Data\_in* is transferred to *A\_count*
- When *Count* = 1, circuit behaves as counter
- If both control inputs are 0, clock pulses do not change the state of the register.
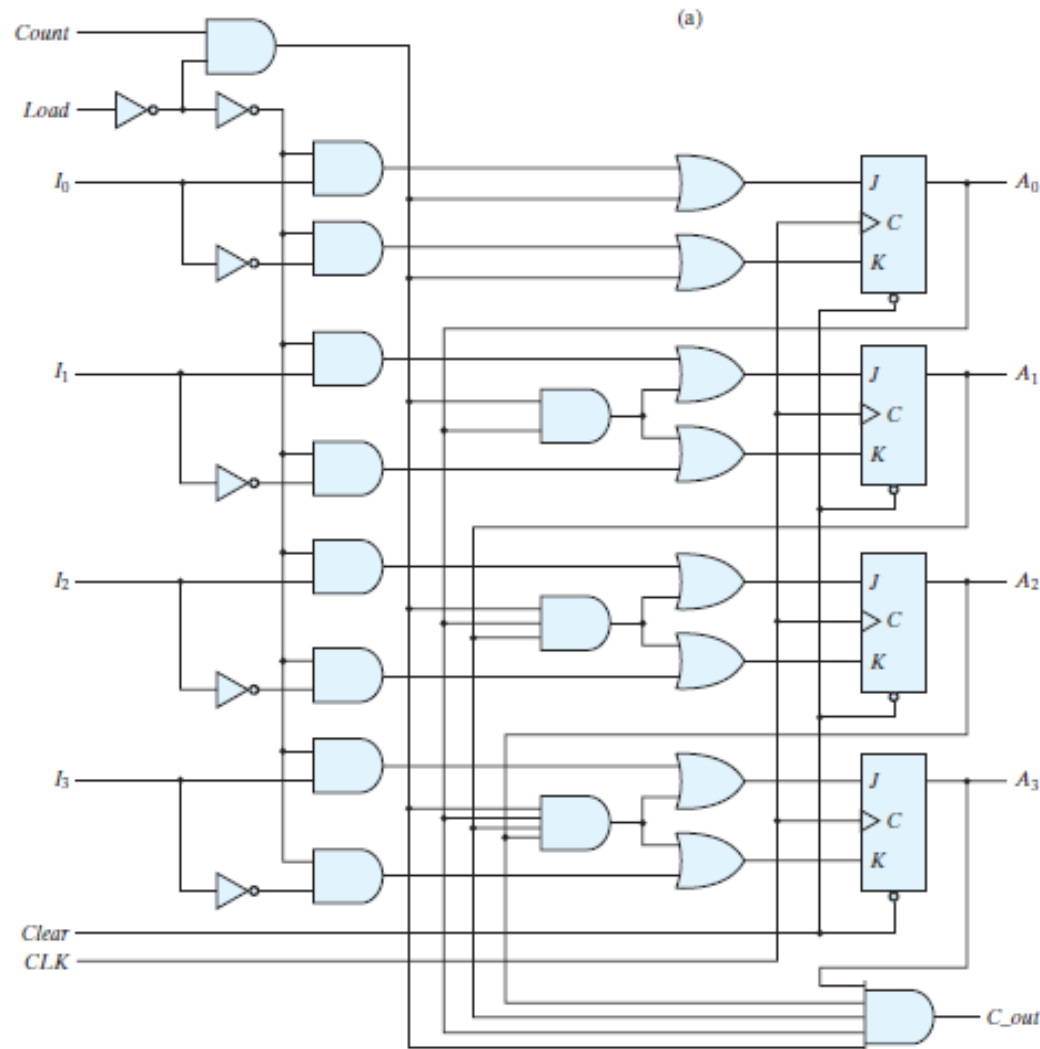
# Binary Counter with Parallel Load: Implementation



Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change



- The carry output becomes a 1 if all the flip-flops are equal to 1 while the count input is enabled.
- This is the condition for complementing the flip-flop that holds the next significant bit.
- The carry output is useful for expanding the counter to more than four bits.

# Binary Counter with Parallel Load: Application
  
## Problem:

Implement a **BCD counter** by modifying the counter with a parallel load shown alongside.

**BCD Counter:** counts from 0000 to 1001 and then back to 0000.




- When the output reaches the count of 1001, both  $A_0$  and  $A_3$  become 1, making the output of the AND gate equal to 1.
- This condition activates loads 0000 on the next clock edge


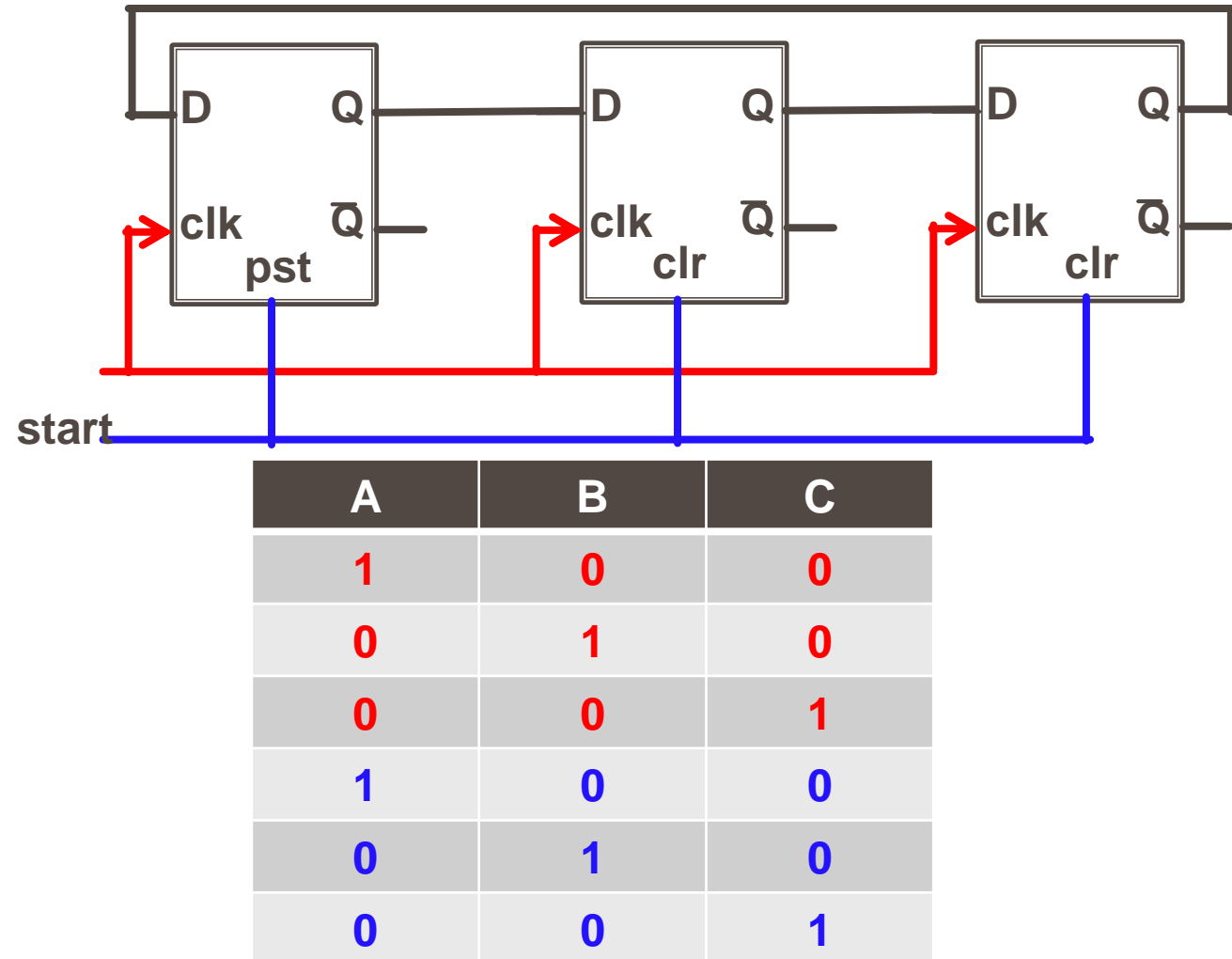
# Ring Counter: Functionality

- A ring counter is a circular shift register with only one flip-flop being set at any particular time; all others are cleared.
- The single bit is shifted from one flip-flop to the next to produce the sequence of timing signals.

- For a four-bit ring counter, the states would be 1000, 0100, 0010 and 0001.



# Ring Counter: Four bit


 
 


- **Modulus of a counter:** Number of the states that the counter counts before repeating itself

- **Ring counter:** Can be used to implement counter of any modulus



# Ring Counter: Using decoder

   

# Johnson Counter: Functionality

---


## Ring Counter:

- N-flip flops have N states (mod N counter)
- For a four-bit ring counter, the states would be 1000, 0100, 0010 and 0001.

## Johnson Counter:

- N-flip flops have  $2N$  states (mod  $2N$  counter)
- Obtained by switch-tail ring counter configuration
- Shift register with the complemented output of the last flip-flop connected to the input of the first flip-flop
- For four flip-flop Johnson counter there will be eight states

# Johnson Counter: Four bits

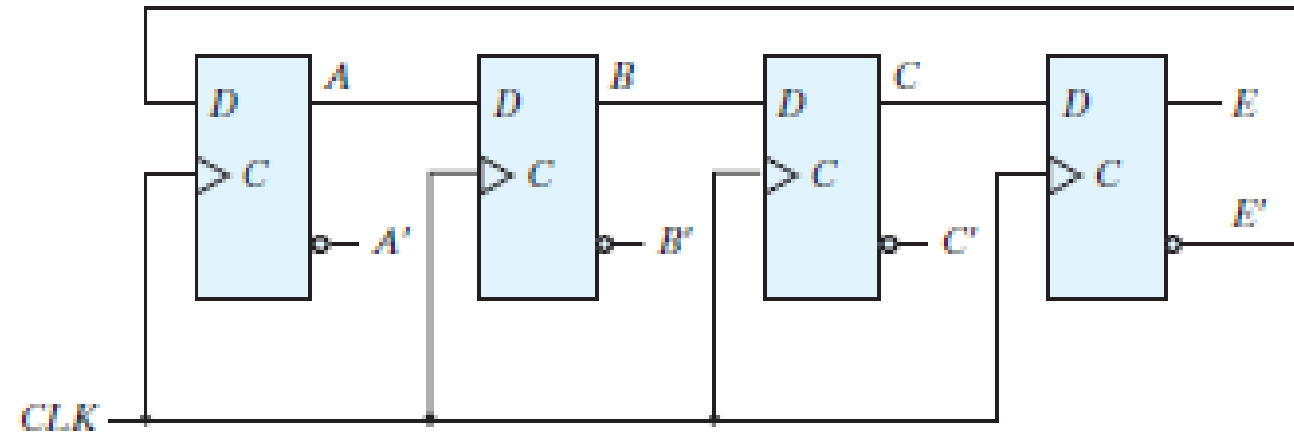


Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	$AB'$
3	1	1	0	0	$BC'$
4	1	1	1	0	$CE'$
5	1	1	1	1	$AE$
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

- Each gate is enabled during one particular state sequence

- An N-bit Johnson counter can be used to provide outputs for 2N timing signal (using 2N decoding gates)

# Johnson Counter: Problem-1

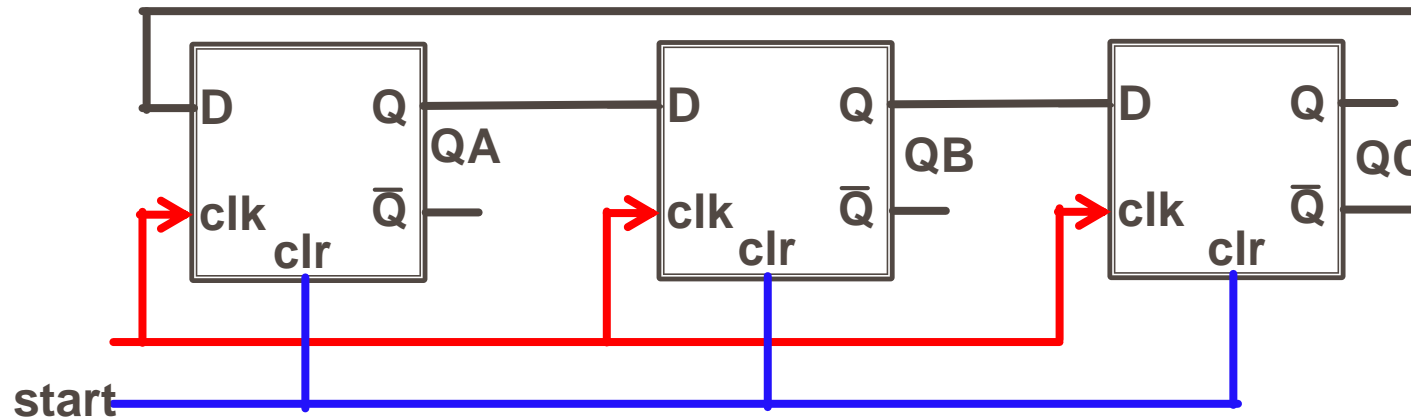


## Problem:

Starting with the state  $\{0,0,0\}$  at 0<sup>th</sup> clock cycle, find the states in subsequent clock cycles.

QA	QB	QC
0	0	0
1	0	0
1	1	0
1	1	1
0	1	1
0	0	1
0	0	0
1	0	0
1	1	0
1	1	1
0	1	1
0	0	1
0	0	0

# Johnson Counter: Frequency divider

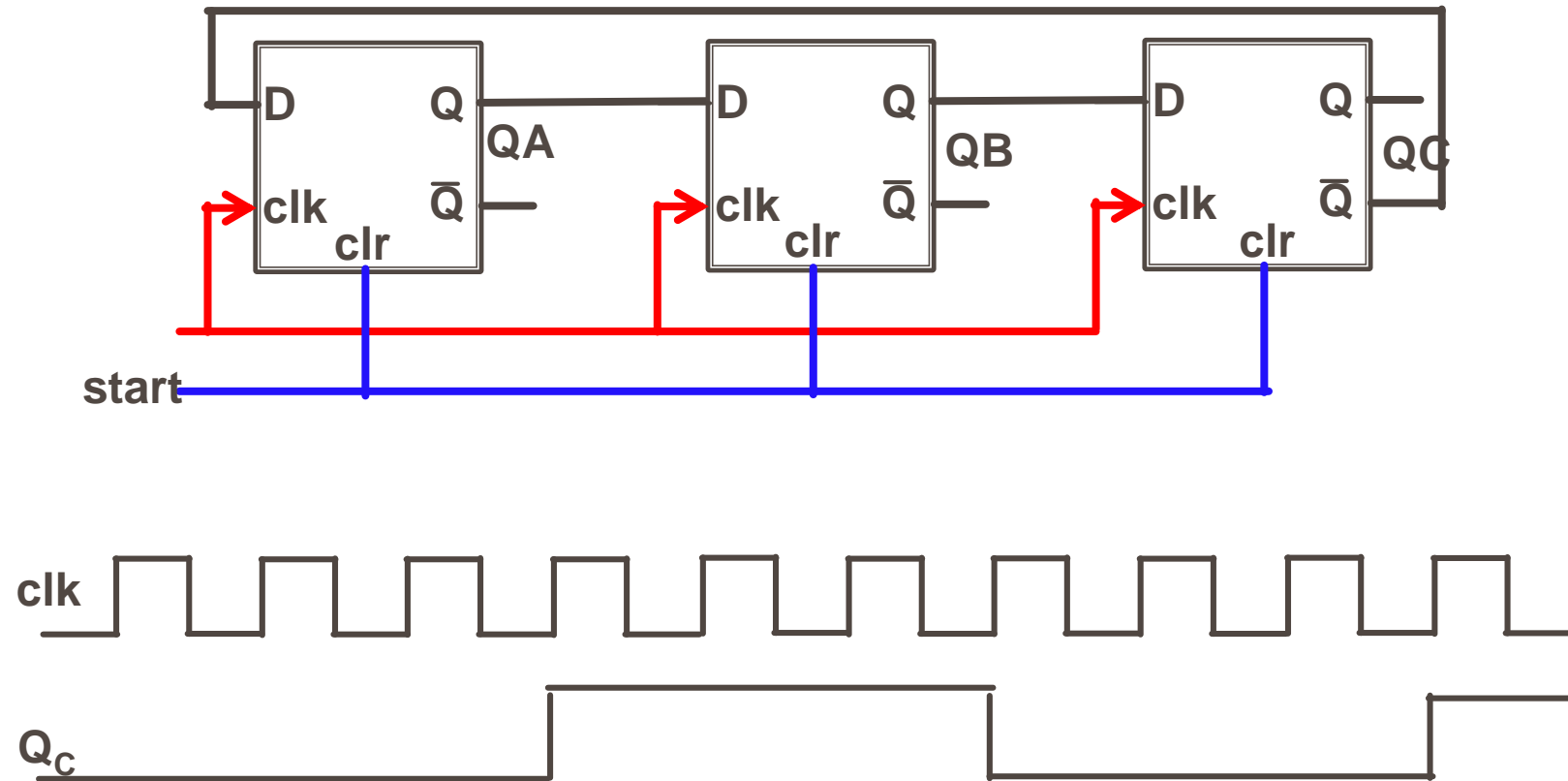

$$F_0 = F_{clk}/6$$

QA	QB	QC
0	0	0
1	0	0
1	1	0
1	1	1
0	1	1
0	0	1
0	0	0
1	0	0
1	1	0
1	1	1
0	1	1
0	0	1
0	0	0