



# DIGITAL CIRCUITS

## Week-14, Lecture-2 Sequential Circuits

Sneh Saurabh  
14<sup>th</sup> November, 2018




# Digital Circuits: Announcements/Revision

---



---

# Sequential Circuits

 



Pipelining

---

---

# Timing constraints on Flip-flops due to delay

# Flip-flop: Constraints

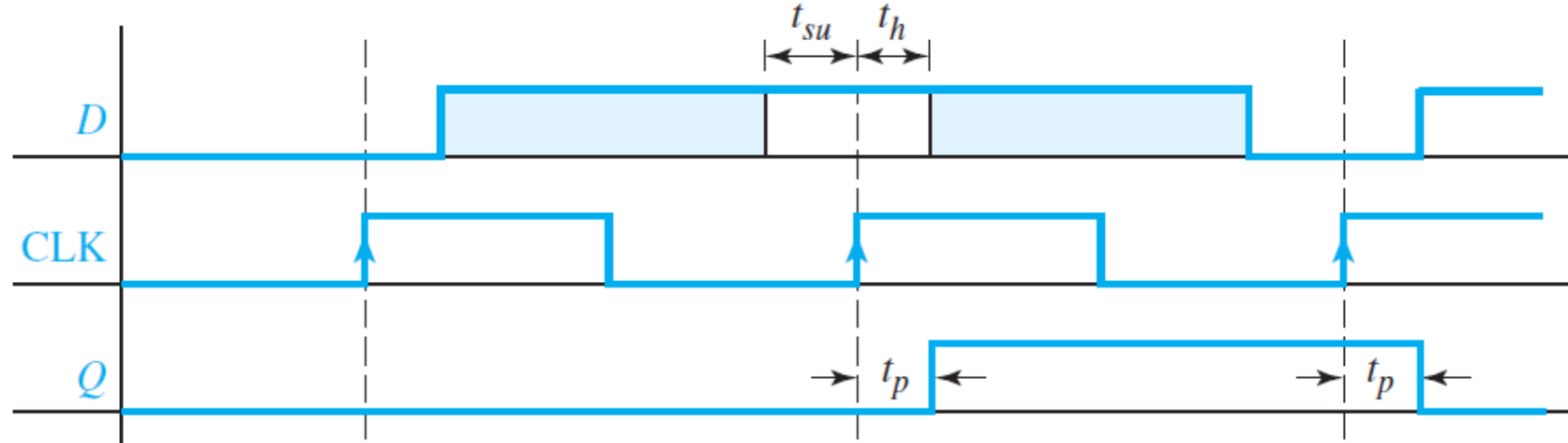 


## Constraints:

- a) **Setup Time ( $t_{su}$ ):** amount of time that  $D$  must be stable before the active edge.
- b) **Hold Time ( $t_h$ ):** amount of time that  $D$  must hold the same value after the active edge

## Delay:

**Clock-to-Q propagation delay ( $t_p$ ):** the amount of time elapsed between the clock changes until the Q output changes.



# Flip-flop: Origin of Setup Time

 

## Setup Time ( $t_{su}$ ):

- Amount of time required for data at  $D$  to propagate through master latch and get sampled by the slave latch
- Setup time decided by the delay of the master latch
- Time interval before the positive edge of clock that the signal on the  $D$  input must be stable
- If the input is changed during this time, the output of the slave latch becomes unpredictable


# Flip-flop: Origin of Hold Time

  

## Hold Time ( $t_h$ ):

- When Clock goes from Low to High, then (due to delay of inverter) for a short duration both latches are enabled
- If the input changes during this time, we don't know whether output corresponds to previous input or present input (unpredictable)
- This is called hold time: time after the active clock edge during which the input must be stable
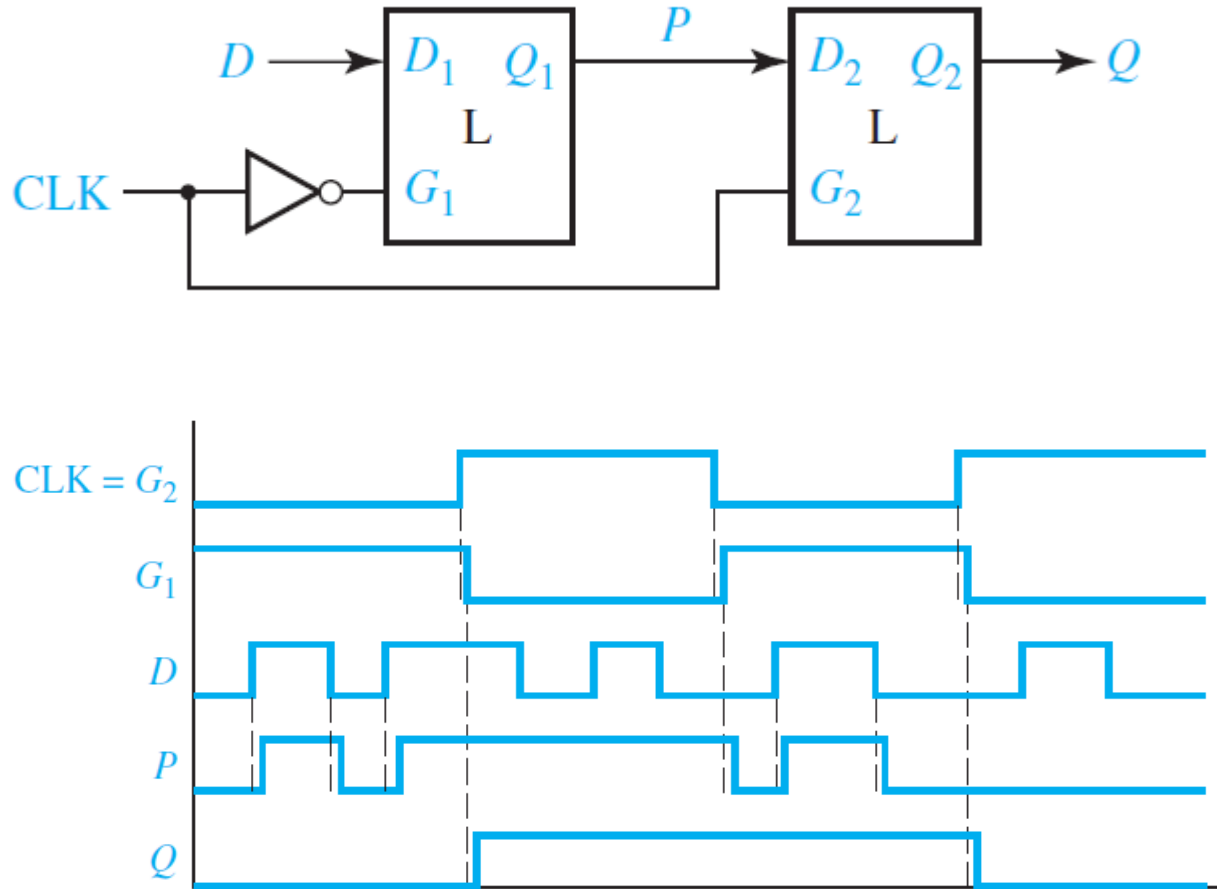
# Flip-flop: Origin of Clock-to-Q propagation delay




## Clock-to-Q propagation delay ( $t_p$ ):


- When active edge of clock appears at the slave latch, it takes time for the data to propagate from  $D_2$  to  $Q$
- This decides the Clock-to-Q propagation delay
- It is also denoted as  $t_{clk-out}$



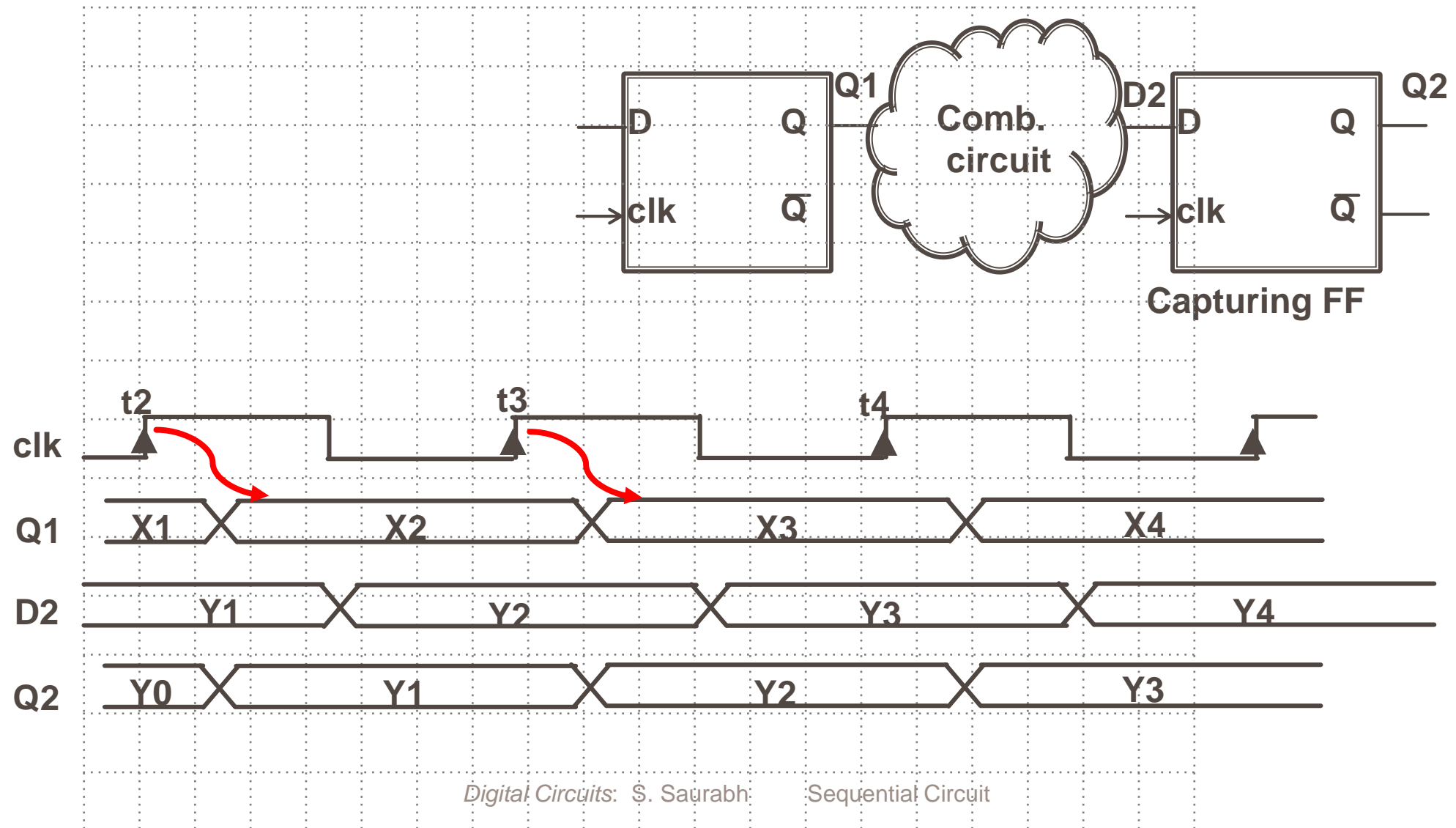
# Constraints on Sequential Circuit: Setup Constraint (1)


 
# Constraints on Sequential Circuit: Setup Constraint (2)


 
# Constraints on Sequential Circuit: Setup Constraint (3)



$$T_{clk} \geq T_{clk-out} + T_{pmax} + T_{setup} + T_{skew}$$


## Clock Skew ( $T_{skew}$ ):

- Difference in arrival time of the active clock edge at launch flip-flop ( $t_{c-launch}$ ) and capture flip-flop ( $t_{c-capture}$ )
- $T_{skew} = t_{c-launch} - t_{c-capture}$

- If active edge of clock arrives late at the launch flip-flop then the effect is similar to adding delay on the launching data
- The effect is opposite if clock arrives late at the capture flip-flop (more time is allowed for data to propagate)

# Constraints on Sequential Circuit: Setup Constraint (4)

---

 

$$T_{clk} \geq T_{clk-out} + T_{pmax} + T_{setup} + T_{skew}$$

How to reduce  $T_{clk}$  or increase the frequency of operation?

- Reduce  $T_{pmax}$ ,  $T_{clk-out}$  or  $T_{setup}$

# Constraints on Sequential Circuit: Setup Constraint (5)


## Problem:

The critical path for a circuit is shown alongside. Find the maximum clock frequency that this circuit can work.

For launch flip-flop:  $T_{setup} = 10\text{ ps}$ ,  $T_{clk-q} = 20\text{ ps}$ ,

For capture flip-flop:  $T_{setup} = 30\text{ ps}$ ,  $T_{clk-q} = 25\text{ ps}$

 $T_{launch} = 140\text{ ps}$   $T_{capture} = 90\text{ ps}$   $T_{data} = 400\text{ ps}$



## Answer:

$$T_{period} > T_{clk-q} + T_{data} + T_{setup} + (T_{launch} - T_{capture})$$

$$T_{period} > 20 + 400 + 30 + 140 - 90$$

$$T_{period} > 500\text{ ps} \Rightarrow f_{clk} < 2\text{ GHz}$$