



DIGITAL CIRCUITS

Week-10, Lecture-2 Sequential Circuits


Sneh Saurabh
10th October, 2018



Digital Circuits: Announcements/Revision




Sequential Circuits

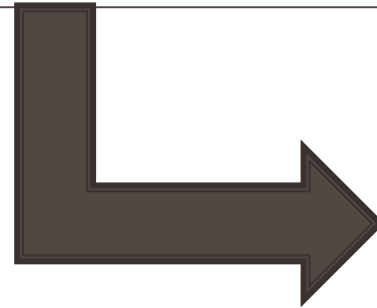

Latches

SR Latch: Basics

 


Can you derive function table for an SR Latch?

- **Set State:** When output $Q = 1$ and $Q' = 0$
- **Reset State:** When $Q = 0$ and $Q' = 1$
- Outputs Q and Q' are normally the *complement* of each other

S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

SR Latch: Normal operation (Set State)

 


S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1 (forbidden)

- Under normal conditions $S = R = 0$ unless the state has to be changed

Reaching Set State:

- The application of a momentary $S = 1$ causes the latch to go to the **set state**
 - Then $S = 0$ is made before any other changes take place, to avoid forbidden input condition ($S = R = 1$)
 - When S goes back to 0, the latch still remains in the set state (**memory action**)

SR Latch: Normal operation (Reset State)

 


Reaching Reset State:

- After $S = R = 0$, it is possible to go to the **reset state** by momentarily applying a $R = 1$
- Then $R = 0$ is made, and the latch still remains in the reset state

S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1 (forbidden)

- When $S = R = 0$, the latch can be in either the set or the reset state, depending on **which input was most recently a 1**

SR Latch: Forbidden State

 


S	R	Q	Q'
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$)
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$)
1	1	0	0 (forbidden)

Forbidden state:

- When $S = R = 1$, $Q = Q' = 0$
 - Both outputs are equal to 0 (rather than be mutually complementary)
- **Race condition:** In the forbidden state, if both inputs are switched to $S = R = 0$ simultaneously, the device will enter an unpredictable or undefined state
- In practical applications, setting both inputs to 1 is forbidden



SR Latch: Active Low

 


Can you derive function table for an NAND-based SR Latch?

- Input signals for the NAND-based latch requires the complement of those values used for the NOR-based latch
- Because the NAND latch requires a 0 signal to change its state, it is sometimes referred to as an $S'R'$ latch or $\bar{S}\bar{R}$ latch (primes indicate active low)

S	R	Q	Q'
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$)
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$)
0	0	1	1 (forbidden)

  

D Latch (Transparent Latch): Basics

 

- Most widely used latch is D latch for circuit applications
- Eliminates reaching forbidden state in the SR latch by ensuring that inputs S and R are never equal to 1 at the same time

Can you derive function table for an SR Latch with Enable?

S	R	Q	Q'
1	0	0	1
1	1	0	1
0	1	1	0
1	1	1	0
0	0	1	1


(after $S = 1, R = 0$)

(after $S = 0, R = 1$)

(forbidden)

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

 
D Latch (Transparent Latch): Functionality



En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state


- The D latch holds data in its internal storage
 - The binary information present at the data input of the D latch is transferred to the Q output when the enable input is asserted.
 - **Transparent latch:** The output follows changes in the data input as long as the enable input is asserted
-
- When $En = 0$, the binary information that was present at the data input at the time the transition occurred is retained (i.e., stored) at the Q output [**Memory Action**]

 D Latch (Transparent Latch): Illustration




D

<i>En</i>	<i>D</i>	Next state of <i>Q</i>
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

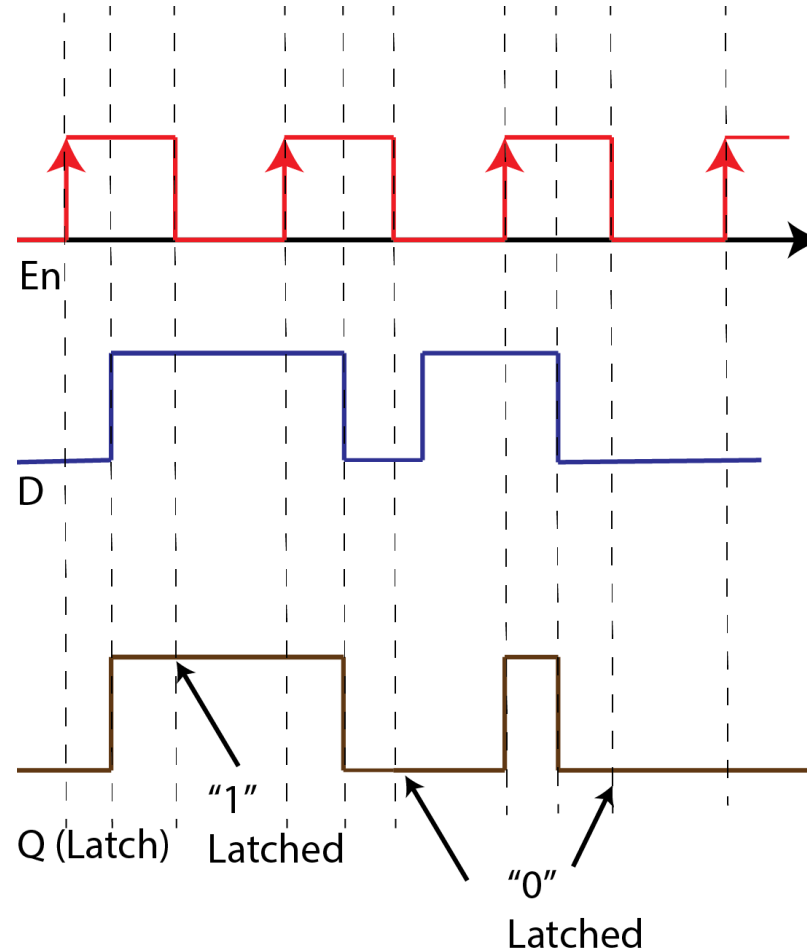

D Latch (Transparent Latch): Active Low Enable

 - An inverter can be placed before the En pin
- D Latch is enabled when $En = 0$



Problem: Assuming that the latch is active low enabled, draw the waveform at the Q-pin of the D latch

