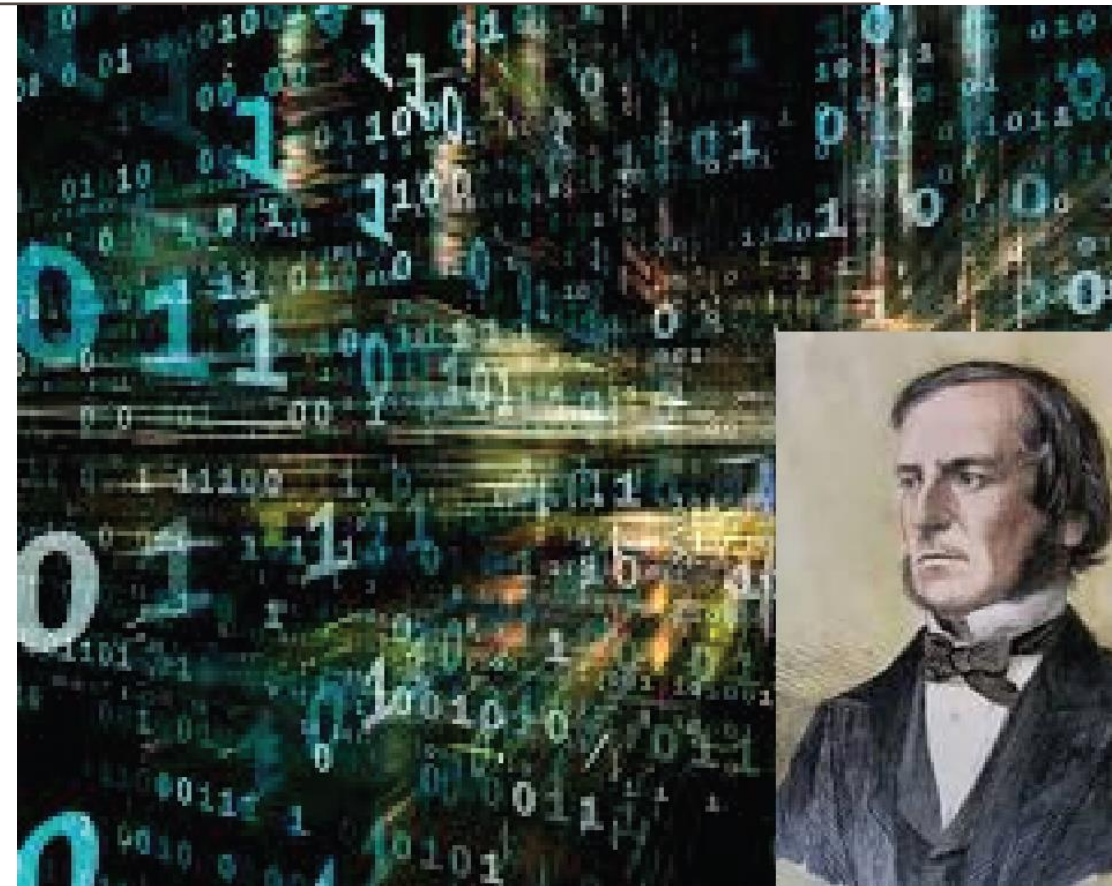




# DIGITAL CIRCUITS

## Week-9, Lecture-2 Combinational Circuits

Sneh Saurabh  
5<sup>th</sup> October, 2018



# Digital Circuits: Announcements/Revision


---



---


---

# Adder/Subtractor

 

## Improving Speed
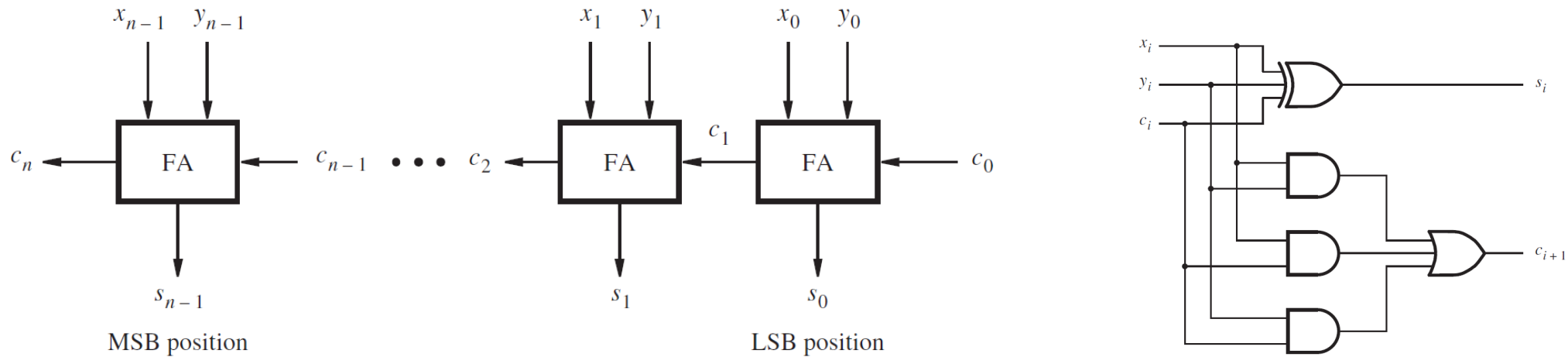
# Adder Subtractor Unit: Performance Issues



- For a full-adder the delay for the carry-out signal is equal to two gate delays
- The longest delay is along the carry computation path
  - Computation of  $c_n$  requires that  $c_{n-1}$  is computed,  $c_{n-1}$  waits for  $c_{n-2}$  and so on

- For  $n$ -stage ripple carry adder, there is  $(2n + 1)$  gate delays
- When  $n = 32$  or  $n = 64$ , the delay becomes unacceptably high
- **Fast adder circuit is required: computation of carry must be speeded**

# Generate and Propagate Functions

- $c_{i+1} = x_i y_i + x_i c_i + y_i c_i$
- $c_{i+1} = x_i y_i + (x_i + y_i) c_i$
- $c_{i+1} = g_i + p_i c_i$

where  $g_i = x_i y_i$  and  $p_i = (x_i + y_i)$

## Generate function:

- The function  $g_i$  is equal to 1 when both inputs  $x_i$  and  $y_i$  are equal to 1 (regardless of the value of the incoming carry to this stage  $c_i$ )
- Since in this case stage  $i$  is guaranteed to generate a carry-out,  $g$  is called the **generate function**

## Propagate function:

- The function  $p_i$  is equal to 1 when at least one of the inputs  $x_i$  and  $y_i$  is equal to 1
  - In this case a carry-out is produced if  $c_i = 1$
  - The effect is that the carry-in of 1 is propagated through stage  $i$
  - Hence  $p_i$  is called the **propagate function**
- 
- Both *generate* and *propagate* functions  $g_i$  and  $p_i$  can be computed by a single level of gate AND/OR
  - For computing  $g_i$  and  $p_i$  information from other stages are not required

# Carry lookahead adder

- $c_{i+1} = g_i + p_i c_i$  where  $\mathbf{g_i = x_i y_i}$  and  $\mathbf{p_i = (x_i + y_i)}$

Expanding  $c_i = g_{i-1} + p_{i-1} c_{i-1}$

$$c_{i+1} = g_i + p_i (g_{i-1} + p_{i-1} c_{i-1})$$

Expanding  $c_{i-1}, c_{i-2}$  till  $c_0$

$$\mathbf{c_{i+1} = g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + \dots + p_i p_{i-1} \dots p_2 p_1 g_0 + p_i p_{i-1} \dots p_1 p_0 c_0}$$


- Computation of  $c_{i+1}$  requires only two-levels (one AND and one OR)
- Computation of carry is very fast (computation of  $c_{i+1}$  does not wait for  $c_i$ )
- Adder based on this equation of carry is known as carry-lookahead adder (CLA)

# Carry lookahead adder

- $c_0 = \text{Input Carry}$
- $c_1 = g_0 + p_0 c_0$
- $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$
- $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$

Carry bit computation requires two level only

 - One gate delay for all generate/propagate signal
- Two gate delays for AND/OR operation
- Therefore, carry bit computation takes 3 gate delays for all the stages (irrespective of number of bits)
- Key to improvement is the fast computation of carry bits



# Propagate Functions: In terms of XOR

- $c_{i+1} = x_i y_i + x_i c_i + y_i c_i$

where  $g_i = x_i y_i$  and  $p_i = (x_i + y_i)$

- Propagate function can also be written as:

$$p_i = (x_i \oplus y_i)$$


- Carry function written in the form of OR gate or XOR gate are **equivalent**
- $c_{i+1} = x_i y_i + (x_i + y_i) c_i \equiv x_i y_i + (x_i \oplus y_i) c_i$



---

---

# Arithmetic Operations

 

Multiplication

# Multiplication: by $2^i$

- How to multiply a binary number by  $2^i$  (i.e. 2, 4, 8, 16, ...)?

- Shift the number left ' $i$ ' times and fill the number with 0 in LSB

- Assume the number is:  $B = b_{n-1}b_{n-2} \dots b_1b_0$

$$2 \times B = b_{n-1}b_{n-2} \dots b_1b_00$$

$$4 \times B = b_{n-1}b_{n-2} \dots b_1b_000$$

....

- Assume:  $B = (1001)_2 = (9)_{10}$

$$2 \times B = (10010)_2 = (18)_{10}$$

- Assume:  $B = (10111)_2 = -(9)_{10}$

$$2 \times B = (101110)_2 = -(18)_{10}$$

- This is correct for both unsigned and signed numbers
- Number of bits in the given number increases

# Division: by $2^i$

- How to divide a number by  $2^i$  (i.e. 2, 4, 8, 16, ...)?

- Shift the number right ' $i$ ' times and fill the left-most bit with the **sign bit**

- Assume the number is:  $B = b_{n-1}b_{n-2} \dots b_1b_0$

$$B \div 2 = b_{n-1}b_{n-1}b_{n-2} \dots b_2b_1$$

$$B \div 4 = b_{n-1}b_{n-1}b_{n-1} \dots b_3b_2$$

....

- This is correct for both unsigned and signed numbers
- Number of bits in the given number remains same

- Assume:  $B = (011000)_2 = (24)_{10}$

$$B \div 2 = (001100)_2 = (12)_{10}$$

- Assume:  $B = (101000)_2 = (-24)_{10}$

$$B \div 2 = (110100)_2 = (-12)_{10}$$

# Multiplier: based on shift and add

- Consider multiplication of two 4-bit numbers:  
 $M = m_3m_2m_1m_0$  and  $Q = q_3q_2q_1q_0$
- Need to find the product:  $P = p_7p_6p_5p_4p_3p_2p_1p_0$

$$Q = q_3q_2q_1q_0 = (q_0 + 2 \times q_1 + 4 \times q_2 + 8 \times q_3)$$

$$\begin{aligned} M \times Q &= M \times (q_0 + 2 \times q_1 + 4 \times q_2 + 8 \times q_3) \\ &= (M \times q_0) + (2 \times M \times q_1) + (4 \times M \times q_2) + (8 \times M \times q_3) \end{aligned}$$

- An eight-bit adder is used to compute the *partial product*
- Total product is computed as a sum of partial products

- Partial product  $P = p_7p_6p_5p_4p_3p_2p_1p_0 = 0$  is initialized

- The bit  $q_0$  is examined
  - If  $q_0 = 1$ , then  $M$  is added to the initial partial product, else 0 is added to  $P$

- The bit  $q_1$  is examined
  - If  $q_1 = 1$ , then  $2 \times M$  is added to  $P$ , else 0 is added to  $P$
  - $2 \times M$  is created just by shifting  $M$  one bit position to the left

- If  $q_2 = 1$ , then  $4 \times M$  is added to  $P$
- If  $q_3 = 1$ , then  $8 \times M$  is added to  $P$

- Since single adder is used it is slow

# Multiplication: Method (Unsigned Numbers)

- Multiplication of binary number is performed in the same manner as decimal number

Multiplicand M	(14)	1 1 1 0
Multiplier Q	(11)	× 1 0 1 1
		-----
		1 1 1 0
		1 1 1 0
		0 0 0 0
		1 1 1 0
		-----
Product P	(154)	1 0 0 1 1 0 1 0


Multiplicand M	(11)	1 1 1 0
Multiplier Q	(14)	× 1 0 1 1
		-----
Partial product 0		1 1 1 0
		+ 1 1 1 0
		-----
Partial product 1		1 0 1 0 1
		+ 0 0 0 0
		-----
Partial product 2		0 1 0 1 0
		+ 1 1 1 0
		-----
Product P	(154)	1 0 0 1 1 0 1 0

- Faster multiplier can be built using multiple adders to compute partial products (in the form of an array)

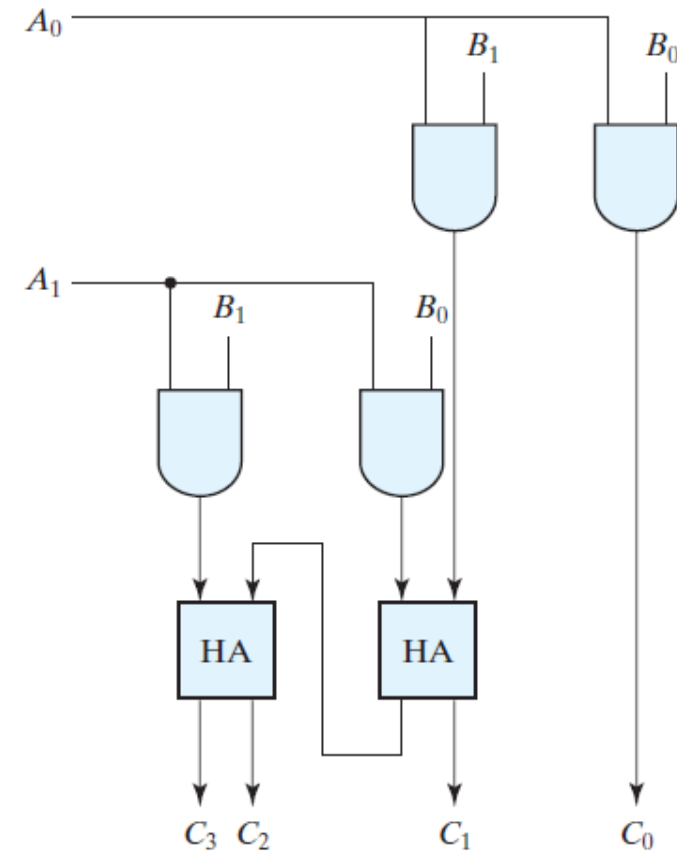
# Multiplication: Array structure ( $2 \times 2$ )

$$\begin{array}{r} \phantom{A_1} B_1 \phantom{B_0} \\ \phantom{A_1} A_1 \phantom{A_0} \\ \hline A_0 B_1 \phantom{A_0 B_0} \\ \phantom{A_1} A_1 B_1 \phantom{A_1 B_0} \phantom{A_1 B_0} \\ \hline C_3 \phantom{C_2} C_2 \phantom{C_1} C_1 \phantom{C_0} \end{array}$$

- Partial products are computed using HA's in this case
- If number of bits is more, then FA's are required


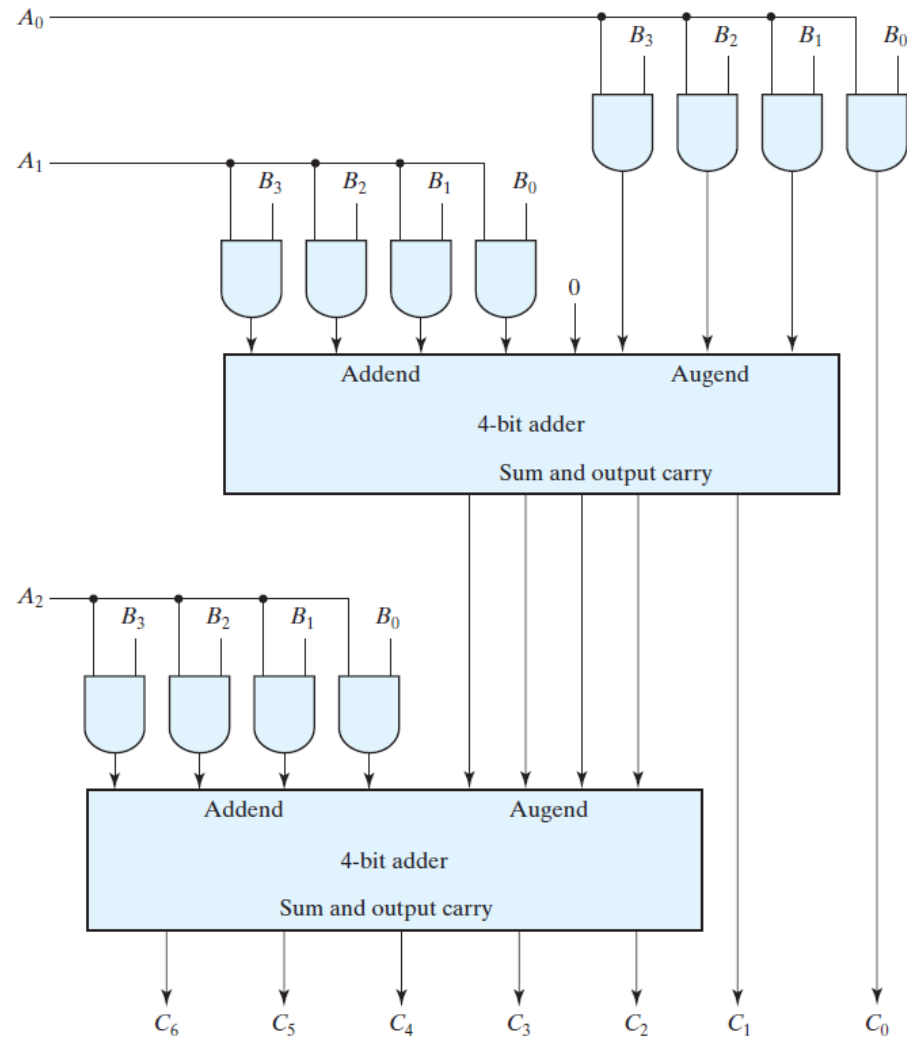
# Multiplication: Array structure ( $4 \times 3$ )



- A bit of the multiplier is AND-ed with each bit of the multiplicand in as many levels as there are bits in the multiplier
- The binary output in each level of AND gates is added with the *partial product of the previous level* to form a new partial product.
- For  $J$  multiplier bits and  $K$  multiplicand bits:
  - $(J \times K)$  AND gates needed
  - $(J - 1) K - \text{bit}$  adders to produce a product of  $(J + K)$  bits.

# Digital Circuits: Practice Problems

Problems 4.10-4.17

from “Digital Design”– M. Morris Mano & Michael D. Ciletti, Ed-5, Pearson (Prentice-Hall).

Problems 5.4, 5.5, 5.7, 5.12, 5.13

from Fundamentals of Digital Logic with Verilog Design - S. Brown, Z. Vranesic

