



# DIGITAL CIRCUITS

## Week-9, Lecture-1 Combinational Circuits

Sneh Saurabh  
3<sup>rd</sup> October, 2018




# Digital Circuits: Announcements/Revision

---



---

# Digital Circuits

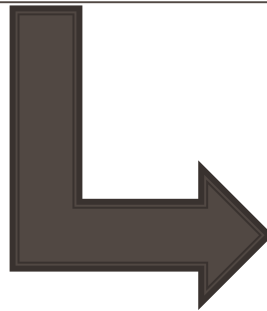

Three-state gates


# Three-states in a digital circuit

---



- **Two states:** conventional logic “0” and “1”

- **Third state:** *high-impedance state*
  - the logic behaves like an **open circuit**, which means that the output appears to be disconnected
  - the circuit connected to the output of the three-state gate is not affected by the inputs to the gate
  - represented as “Z”

# Three-state (Tri-state) buffer

 

$e$	$x$	$f$
0	0	Z
0	1	Z
1	0	0
1	1	1

  

- Realizing logic gates is possible by connecting together the **outputs** of tristate gates (this is known as wired connection)


- This is not possible with ordinary logic gates, because their outputs are always **active**; hence a **short circuit** would occur.

# Priority Encoder: Implementation

---

 **Problem:**


Implement a 2-to-1 MUX using two tri-state buffers and an inverter.



# Priority Encoder: Implementation

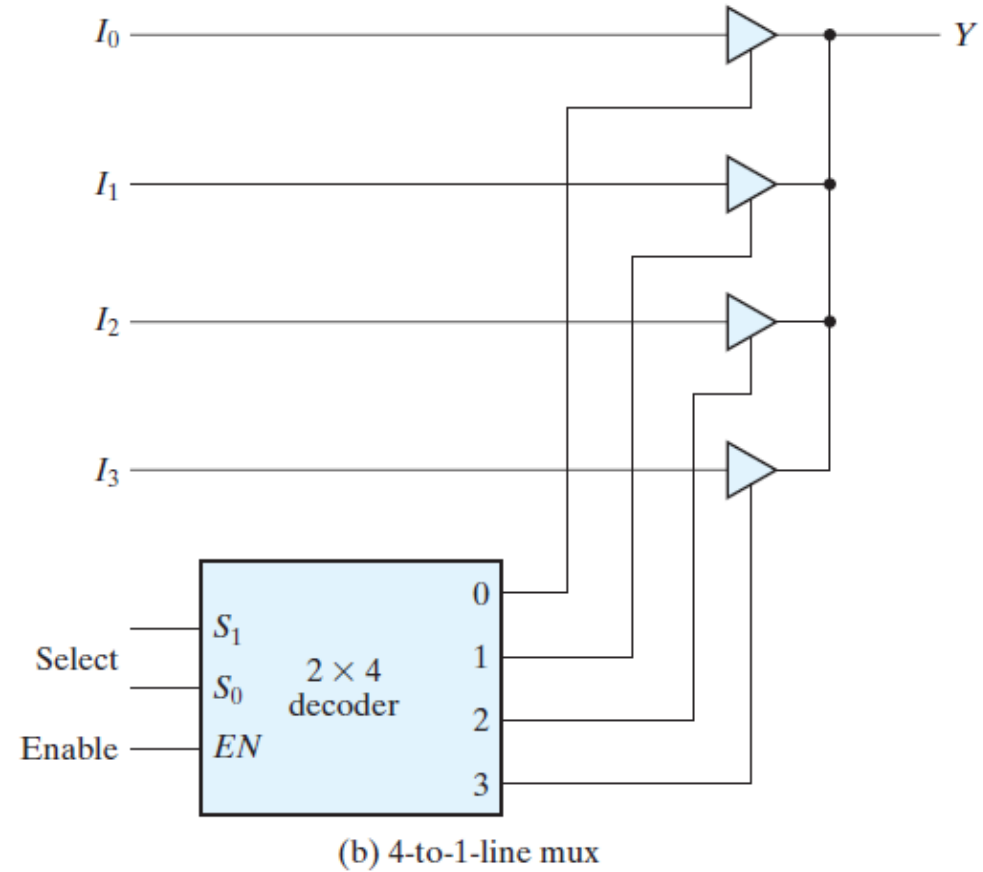
## Problem:

Implement a 4-to-1 MUX using four tri-state buffers and one 2-to-4 decoder.



---

# Digital Circuits

 

## Arithmetic Operations




# Adders: Half Adders and Full Adders (Recap...)

		Carry	Sum
$x$	$y$	$c$	$s$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0



 A circuit which implements the addition of only two bits is known as **Half Adder (HA)**




$c_i$	$x_i$	$y_i$	$c_{i+1}$	$s_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


$$s_i = x_i \oplus y_i \oplus c_i$$

Full Adder Circuit

 


# Adders: Ripple Carry Adder (Recap...)

---

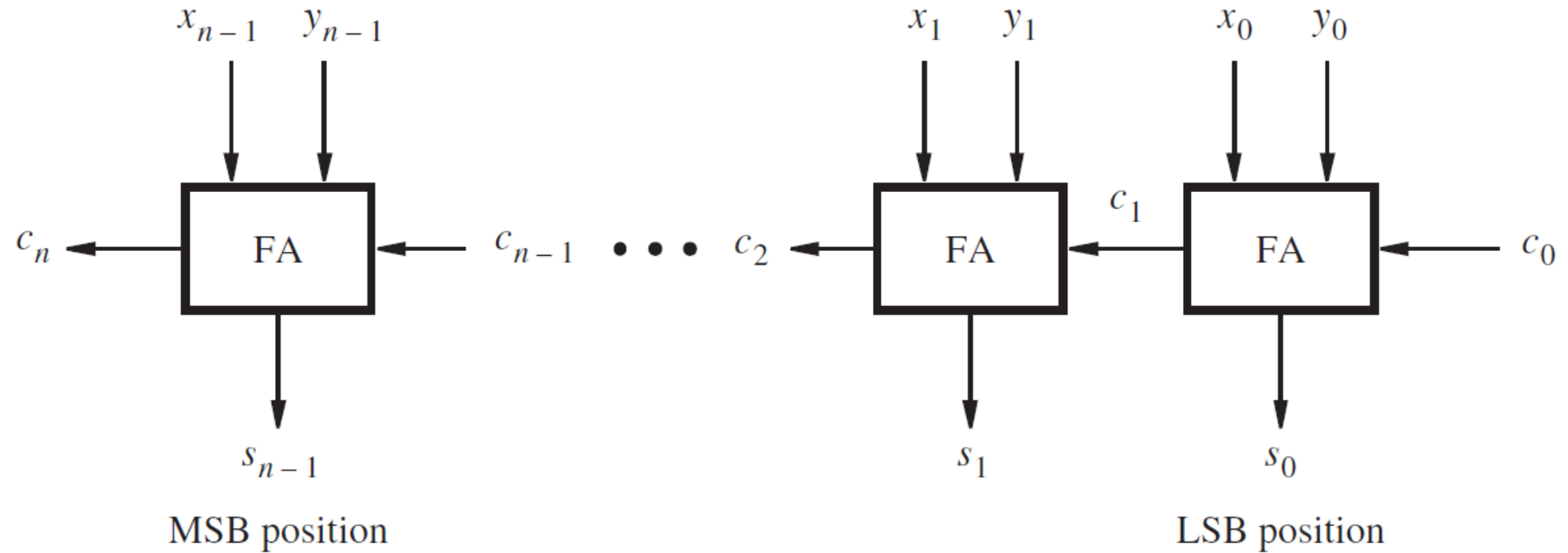
 
# Adders: Adder Subtractor Unit (Recap...)




We will look at two problems of this implementation

1. Arithmetic Overflow
2. Speed

---

---

Adder/Subtractor

 

Arithmetic Overflow

# Arithmetic Overflow: Definition

---

- The result of addition/subtraction is supposed to fit within the significant bits used to represent the numbers
  - For example, if the numbers are represented in 4-bits, then sum/difference of two numbers should also fit in 4-bits
- If  $N$  bits are used to represent signed numbers, then the result must be in the range  $-2^{N-1}$  and  $2^{N-1} - 1$ 
  - For example, if  $N = 4$ , then the result of addition/subtraction should be within  $-8$  to  $+7$ .
- If the result does not fit in this range, then we say that **arithmetic overflow** has occurred.
- To ensure the correct operation of an arithmetic circuit, it is important to be able to detect the occurrence of an arithmetic overflow

# Arithmetic Overflow: Detection

- When sign of numbers are of opposite types, then no overflow can occur
- Take examples of **two 4-bit numbers**, and check under what condition overflow can occur
  - Consider the carry-out from **MSB position ( $c_3$ )** and carry out from **sign-bit position ( $c_4$ )**

$$\begin{array}{r}
 (+7) \quad 0111 \\
 + (+2) \quad +0010 \\
 \hline
 (+9) \quad 1001 \\
 c_4 = 0 \\
 c_3 = 1
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 1001 \\
 + (+2) \quad +0010 \\
 \hline
 (-5) \quad 1011 \\
 c_4 = 0 \\
 c_3 = 0
 \end{array}$$

- Examples suggest that overflow occurs when these carry-outs have different values, and a correct sum is produced when they have the same value

$$\text{➤ } \text{Overflow} = c_3 \oplus c_4$$


$$\begin{array}{r}
 (+7) \quad 0111 \\
 + (-2) \quad +1110 \\
 \hline
 (+5) \quad 10101 \\
 c_4 = 1 \\
 c_3 = 1
 \end{array}$$

$$\begin{array}{r}
 (-7) \quad 1001 \\
 + (-2) \quad +1110 \\
 \hline
 (-9) \quad 10111 \\
 c_4 = 1 \\
 c_3 = 0
 \end{array}$$

- Indeed, this is true in general for both addition and subtraction of 2's-complement numbers.

$$\text{➤ } \text{Overflow} = c_{N-1} \oplus c_N$$


# Arithmetic Overflow: Circuit

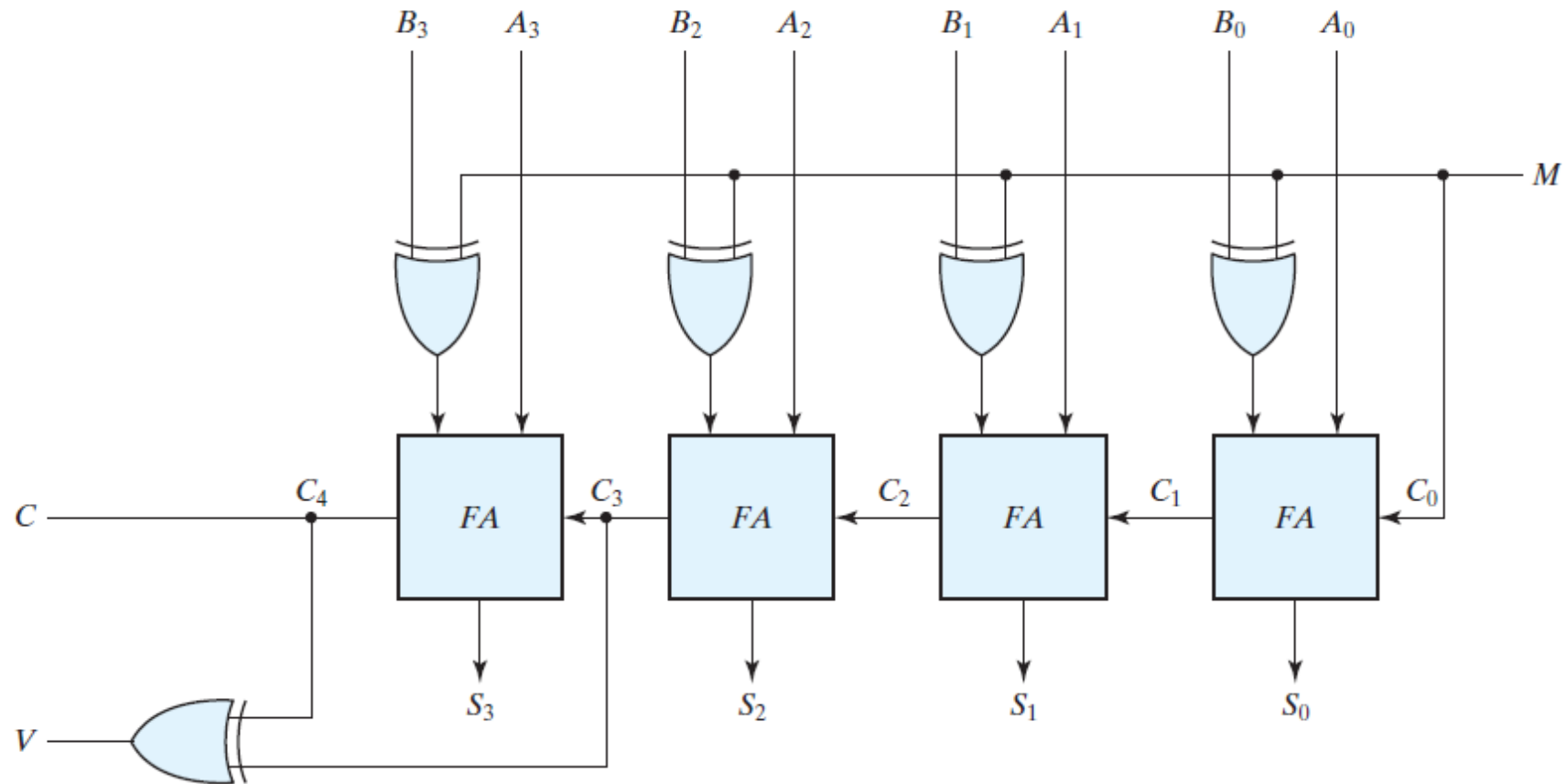

---

---


# Adder/Subtractor

 

## Improving Speed



 
# Adder Subtractor Unit: Performance Issues



- Speed is decided by the largest delay from the time the operands  $X$  and  $Y$  are presented as inputs, until the time all bits of the sum  $S$  and the final carry-out  $c_n$  are valid
- Most of delay is caused by the n-bit ripple-carry adder circuit
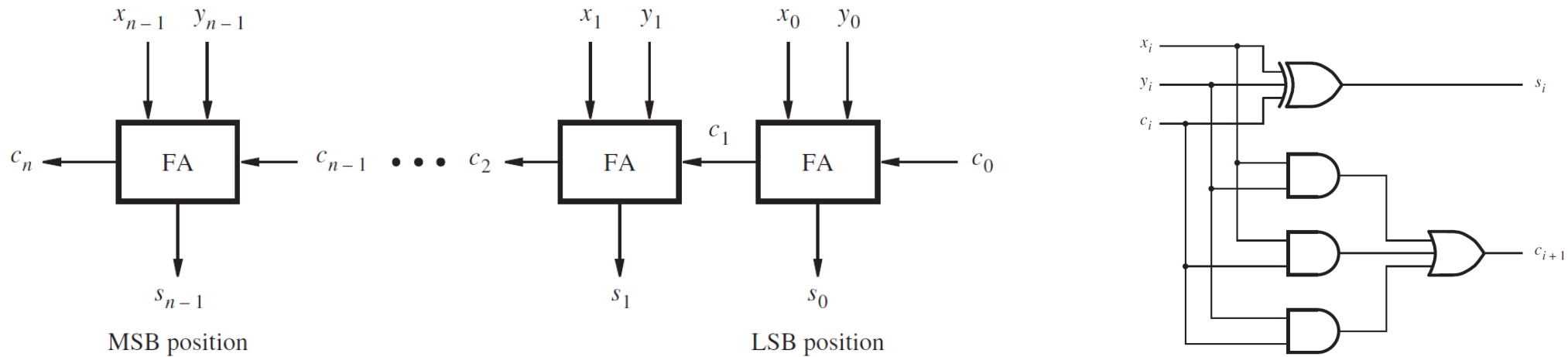
# Adder Subtractor Unit: Performance Issues



- For a full-adder the delay for the carry-out signal is equal to two gate delays
- The longest delay is along the carry computation path
  - Computation of  $c_n$  requires that  $c_{n-1}$  is computed,  $c_{n-1}$  waits for  $c_{n-2}$  and so on

- For  $n$ -stage ripple carry adder, there is  $(2n + 1)$  gate delays
- When  $n = 32$  or  $n = 64$ , the delay becomes unacceptably high
- **Fast adder circuit is required: computation of carry must be speeded**