



DIGITAL CIRCUITS

Week-14, Lecture-1 Sequential Circuits


Sneh Saurabh
13th November, 2018



Digital Circuits: Announcements/Revision



Sequential Circuits

 



Pipelining

Concept of Delay

Delay: Basic concept

- When the input to a logic gate is changed, the output **does not change instantaneously**
- The **transistors** or other switching elements within the gate take a finite time to react to a change in input
 - Time to react depends on electrical characteristics such as **capacitance** and **resistance**
 - The change in the gate output is **delayed** with respect to the input change

Delay: Inverter (Simple model)

  

- For a transition from 1 (High) to 0 (Low), the change in output is delayed by t_{pHL}
 - t_{pHL} is called High to Low **Propagation delay**



- For a transition from 0 (Low) to 1 (High), the change in output is delayed by t_{pLH}
 - t_{pLH} is called Low to High **Propagation delay**

- In general, $t_{pHL} \neq t_{pLH}$
- Sometime average of t_{pHL} and t_{pLH} is specified as propagation delay t_p
- $$t_p = \frac{t_{pHL} + t_{pLH}}{2}$$
- During analysis of a circuit, in this case for both transitions the same propagation delay t_p can be taken



Delay: Timing Diagram

For the circuit shown below, complete the timing diagram.

  Assume that each gate has a propagation delay of 20 ns.



Timing Model: Propagation Delay

  



Low-to-high propagation delay

(t_{pLH}): When the output switches from low-to-high, the time difference between the instant when the output is at 50% of its maximum value and the input is at 50% of its maximum value

High-to-Low propagation delay

(t_{pHL}): When the output switches from high-to-low, the time difference between the instant when the output is at 50% of its maximum value and the input is at 50% of its maximum value

Timing Model: Rise/Fall Time

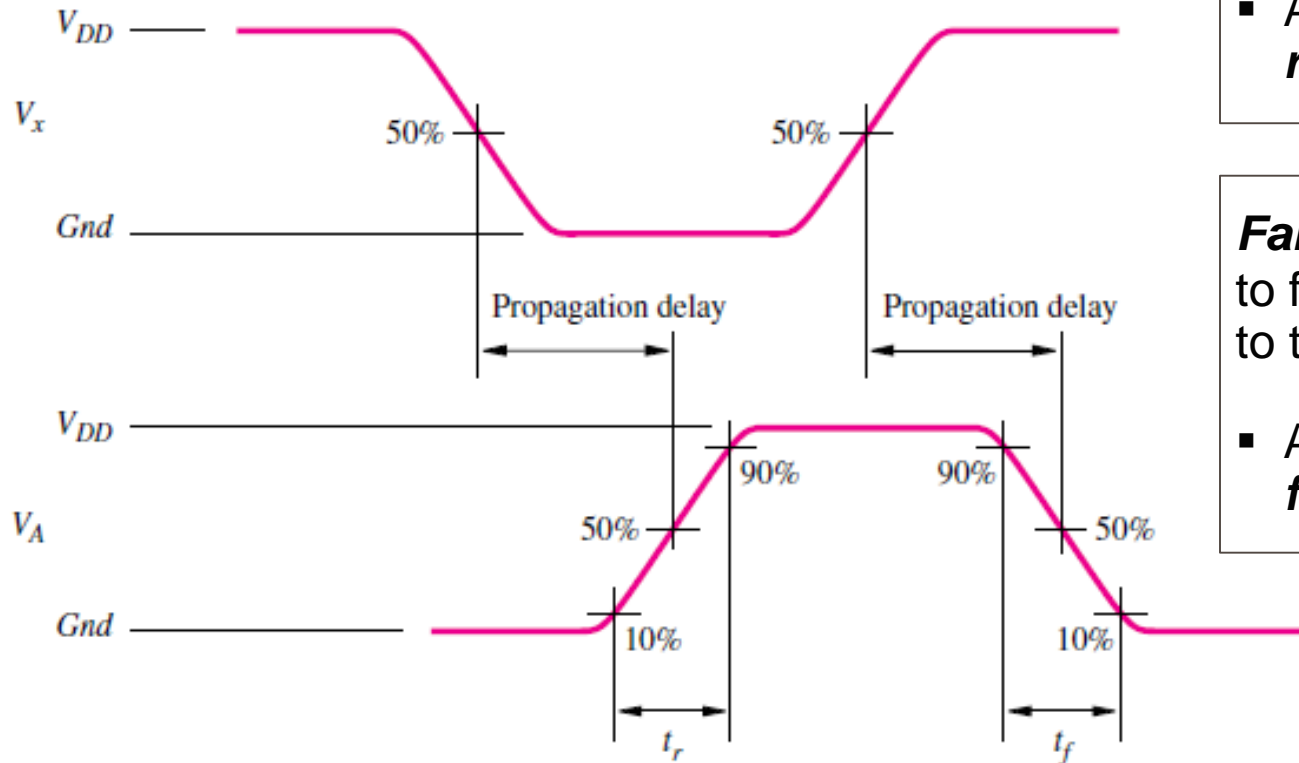 


Rise time (t_r): Time taken by a signal to rise from 10% of its maximum value to the 90% of its maximum value.

- Also called ***rise transition time***, ***rising slew***

Fall time (t_f): Time taken by a signal to fall from 90% of its maximum value to the 10% of its maximum value.

- Also called ***fall transition time***, ***falling slew***



Timing Model: Factors affecting delay

 

Load at the output: If more gates are connected at the output of an inverter or any other logic gate, then the effective capacitance increases.

- As a result, propagation delay will increase

  Fanout (n): Number of other pins driven by the inverter output or output of any other logic gate



Delay in a path in a combinational circuit

Delay in a path in a combinational circuit is computed as a sum of delay in the individual gates.


Problem:

For the circuit shown alongside, it is given that:

Propagation delay of NOT, AND, NOR gates are 1 ns, 6 ns, 3 ns respectively.

Compute the minimum and the maximum delay between the following ports:

 - a) From A to Y
- b) From B to Y
- c) From C to Y





Answer:

- a) From A to Y: min = max = 13 ns
- b) From B to Y: min=9 ns, max=13 ns
- c) From C to Y: min=max=9 ns

Timing constraints on Flip-flops due to delay

Flip-flop: Constraints

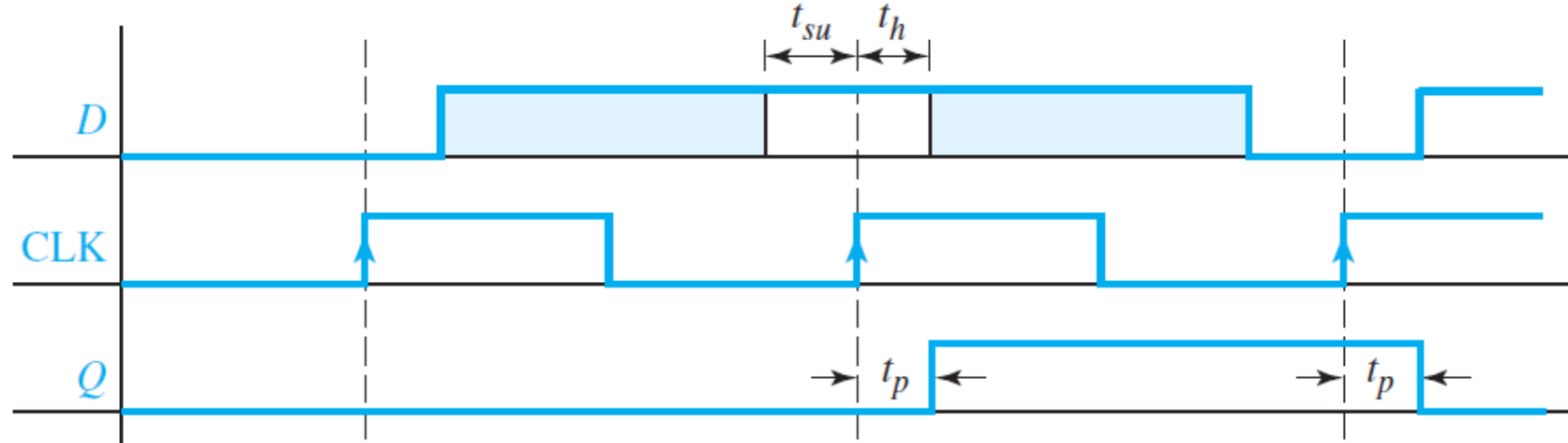 

Constraints:

- a) **Setup Time (t_{su}):** amount of time that D must be stable before the active edge.
- b) **Hold Time (t_h):** amount of time that D must hold the same value after the active edge

Delay:

Clock-to-Q propagation delay (t_p): the amount of time elapsed between the clock changes until the Q output changes.