



# DIGITAL CIRCUITS

## Week-11, Lecture-1 Sequential Circuits

Sneh Saurabh  
23<sup>rd</sup> October, 2018




# Digital Circuits: Announcements/Revision

---




---

# Sequential Circuits

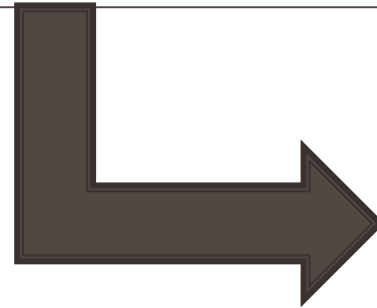

Flip-flops
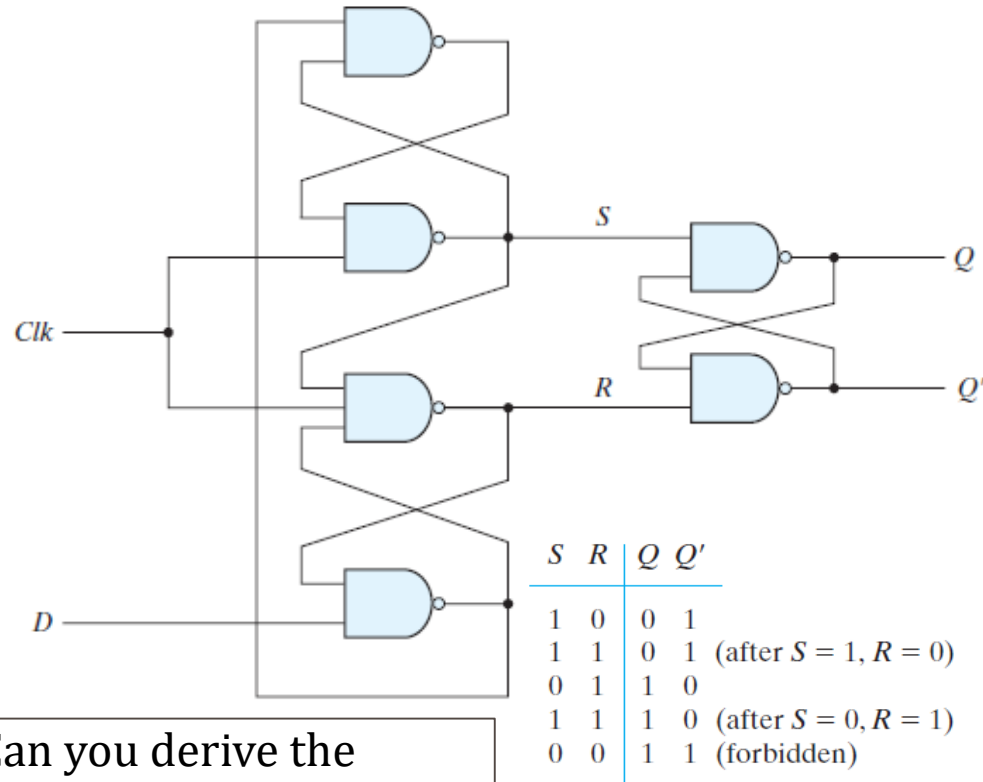
# Flip-flop Implementation: positive edge-triggered (1)




Can you derive the functionality?

**Three SR latches:** Two connected to Clk and D, One connected to the output

- When  $Clk = 0$ , SR latch connected to the output has  $S = R = 1$ , and present state is maintained
  - Input D can be 0 or 1, it will not matter

- When clock changes to  $Clk = 1$ 
  - If  $D = 0$ , R changes to  $R = 0$ , and S remains at  $S = 1$  and  $Q = 0$  state reached
  - If  $D = 1$ ,  $R = 1$  remains, and S changes to  $S = 0$  and  $Q = 1$  state reached
 
# Flip-flop Implementation: positive edge-triggered (2)




## To ensure edge-triggered operation

- At  $Clk = 1$  changes in  $D$  should not be recorded further (only the value of  $D$  when positive edge occurred should decide  $Q/Q'$ )

- At the positive edge  $Clk = 1$ , assume that  $D = 0$ 
  - $S = 1, R = 0$  is reached (as already explained)
  - If now  $D$  changes  $D = 1$ , no impact on the output of the bottom NAND gate
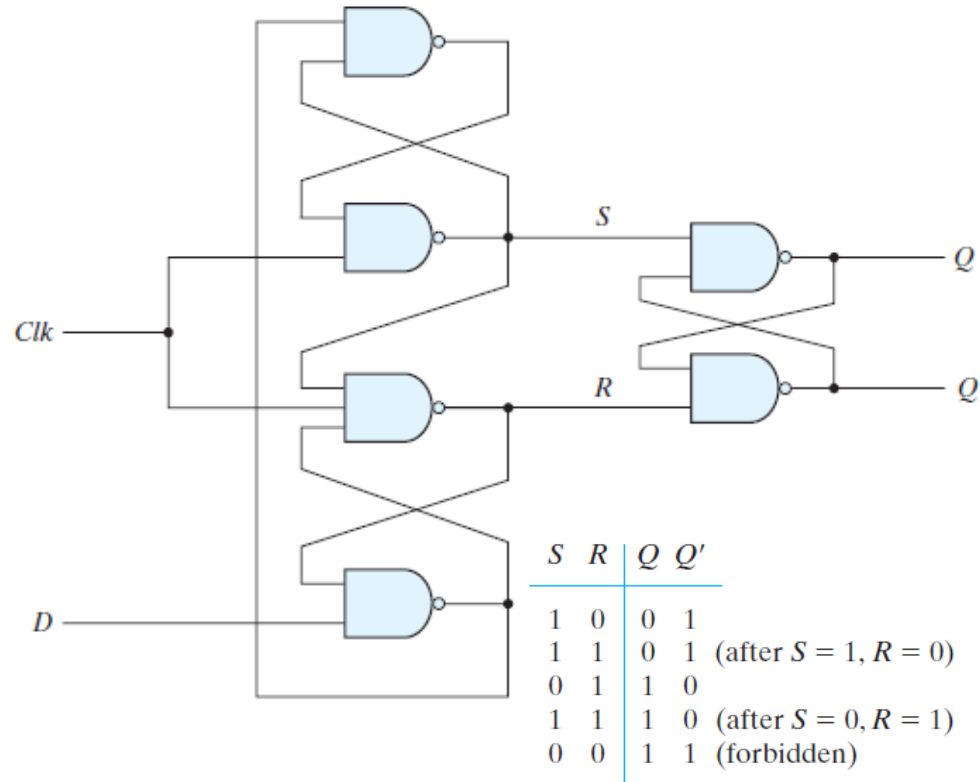
# Flip-flop Implementation: positive edge-triggered (3)



## To ensure edge-triggered operation


- At  $Clk = 1$  changes in  $D$  should not be recorded further (only the value of  $D$  when positive edge occurred should decide  $Q/Q'$ )

- At the positive edge  $Clk = 1$ , assume that  $D = 1$ 
  - $S = 0, R = 1$  is reached (as already explained)
  - If now  $D$  changes to  $D = 0$ , the output of the bottom NAND gate changes from 0 to 1
    - Since  $S = 0, R$  remains at 1, (no impact of this change)
    - Since  $S = 0$ , the output of the top NAND gate remains at 1 (no impact of this change) and  $S$  remains at 0

---

---

# Sequential Circuits

 

Flip-flops  
with  
Clear/Preset

# Flip-flops with Clear/Preset

---

## Clear:

- It takes the flip-flop Q pin to 0
- Also called “Reset”

## Preset:

- It takes the flip-flop Q pin to 1
- Also called “Set”


## Two Types based on when the effect takes place:

- Asynchronous Clear/Preset:
  - The effect of Clear/Preset on Q is observed immediately (without waiting for clock edge)
- Synchronous Clear/Preset
  - The effect of Clear/Preset on Q is observed only when appropriate clock edge arrives



# Flip-flops with Clear/Preset: Asynchronous vs. Synchronous





---

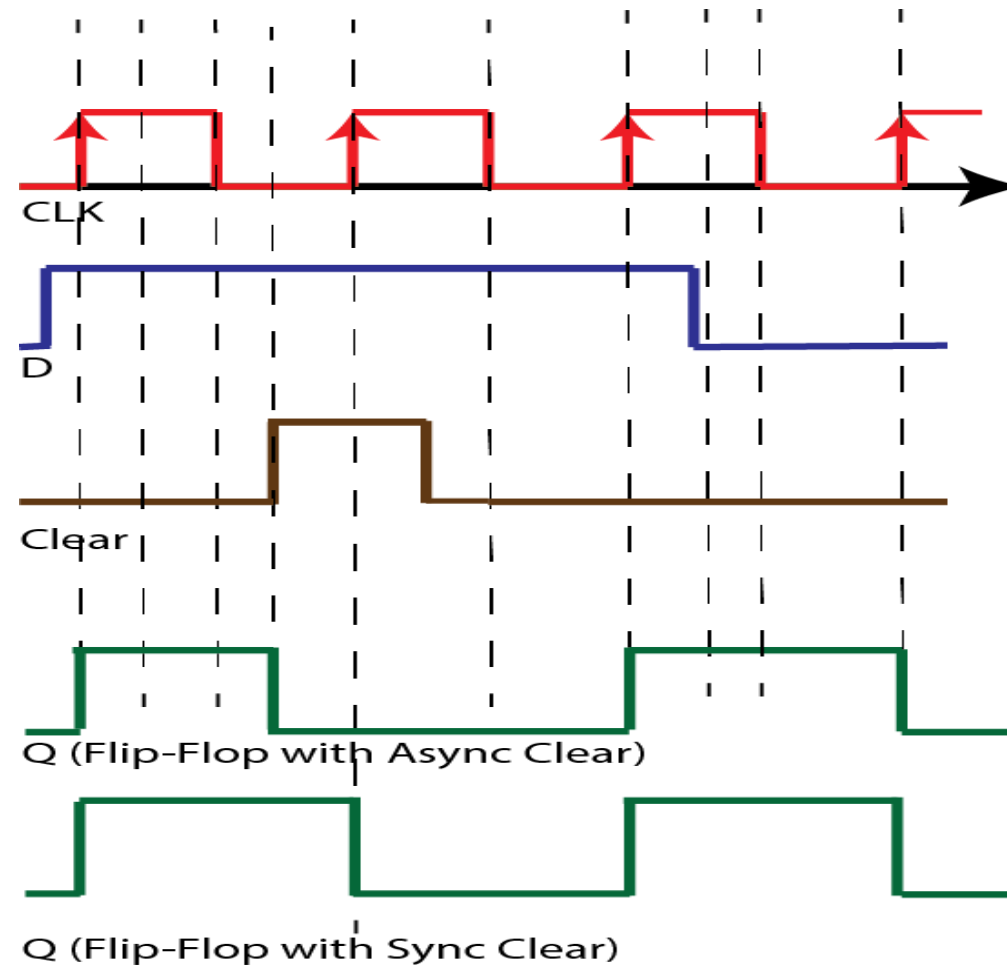


# Flip-flops with Clear/Preset
    
## Two Types based on level :

- Active High Clear/Preset
- Active Low Clear/Preset


 
# Flip-flop with Asynchronous Clear/Preset




## Operation:

- “Reset” or “Clear” is active low in this case
- When  $Reset = 0$ ,  $Q'$  is forced to 1 and  $S$  is forced to 1
- $Q$  changes to 0 immediately, irrespective of Clock

$R$	$Clk$	$D$	$Q$	$Q'$
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0
 
# Flip-flop with Synchronous Clear/Preset




## Operation:

- “Clear” is active high in this case
- When  $\text{Clear} = 1$ , and **Clock edge arrives**,  $Q$  is changes to 0



---

# Sequential Circuits

 

Other types  
of Flip-flops

# JK Flip-Flop using D flip-flop

  

## Problem:


A JK flip-flop is realized using a D flip-flop using the circuit shown alongside.

Obtain the functionality of the JK flip-flop in a form of *characteristics table*.

## Characteristics Table

- A tabular representation of the functionality of a sequential circuit such as a flip-flop
- The **next state** of the circuit is represented as a function of inputs and the **present state**
  - Next State: The state that results after clock transition  $Q(t + 1)$
  - Present State: The state just before the application of clock edge  $Q(t)$


# JK Flip-Flop: Characteristics Table

 
 
## Problem:


A JK flip-flop is realized using a D flip-flop using the circuit shown alongside.

Obtain the functionality of the JK flip-flop in a form of *characteristics table*.



$J$	$K$	$Q(t + 1)$		$J$	$K$	$Q(t + 1)$	<b>Comment</b>
0	0			0	0	$Q(t)$	No change
0	1			0	1	0	Reset
1	0			1	0	1	Set
1	1			1	1	$Q'(t)$	Complement

# JK Flip-Flop: Characteristics Equation

 


## Problem:

A JK flip-flop is realized using a D flip-flop using the circuit shown alongside.

Obtain the functionality of the JK flip-flop in a form of *characteristics equation*

 
## Characteristics Equation

- Representation of the functionality of a sequential circuit such as a flip-flop in the form of an algebraic expression
- $Q(t + 1) = f(inputs, Q(t))$





# JK Flip-Flop: Characteristics Equation

 


## Problem:

A JK flip-flop is realized using a D flip-flop using the circuit shown alongside.

Obtain the functionality of the JK flip-flop in a form of *characteristics equation*

To obtain characteristics equation from circuit

 - Express the function at “D” in terms of inputs and  $Q(t)$



$$Q(t + 1) = JQ' + K'Q$$